


TRIBHUVAN UNIVERSITY  
INSTITUTE OF ENGINEERING  
**Examination Control Division**

2081 Baishakh


Exam.	Back		
Level	BE	Full Marks	80
Programme	BEL, BEX, BEL, BCT, BAM, BIE, BAG, BAS, BCH	Pass Marks	32
Year / Part	I / I	Time	3 hrs.

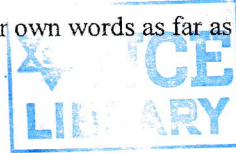**Subject: - Basic Electrical Engineering (EE 401)**


- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.



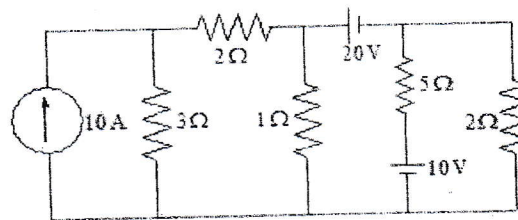
1. a) What do you mean by ideal and practical voltage source? Explain the effect of an internal resistance of a voltage source on its terminal characteristics. [6]
- b) Calculate the temperature at which the resistance of a conductor becomes 20% more than its resistance at 27°C. The values of the temperature coefficient of resistance of the conductor is  $2.0 \times 10^{-4}/^{\circ}\text{C}$ . [5]
- c) Three resistors of value 16  $\Omega$ , 24  $\Omega$  and 32  $\Omega$  are connected in parallel and take a total current of 5.2 A. Find (i) current in each resistor (ii) voltage across the combination. [5]
2. a) Determine the power through 5 $\Omega$  resistor of the circuit given below using Nodal Analysis. [6]



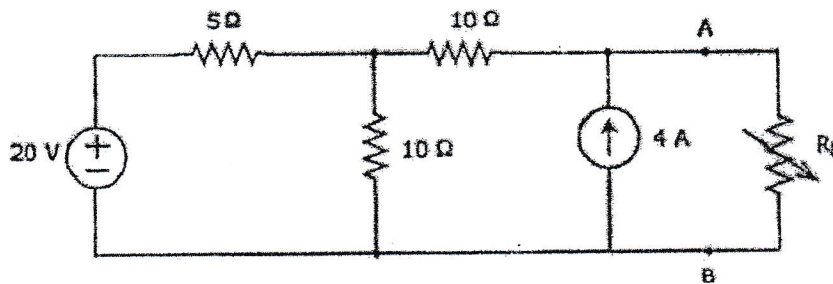
- b) Find the maximum power that can be delivered to the load resistor  $R_L$  of the circuit shown in the following figure. [6]



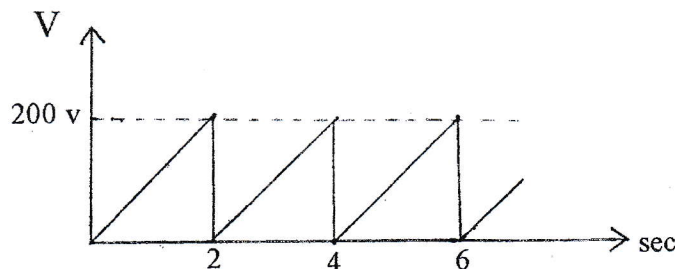- c) State and illustrate superposition theorem. [4]
3. a) Define capacitance in terms of circuit viewpoint, energy viewpoint and geometrical viewpoint. [4]
- b) Find form factor for the voltage wave as shown in figure. [6]



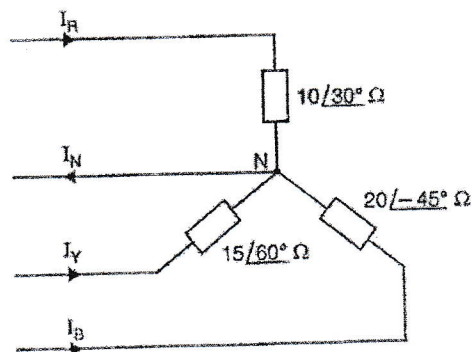- c) Explain voltage – current relationship in pure inductor. Also, illustrate that an inductor does not consume any wattfull power over one cycle of A.C. supply. [6]
4. a) A voltage of  $e(t) = 169.2 \sin 314t$  Volts is applied across series RLC circuit consists of a resistor of 30 ohm, an inductor of 80 mH and a capacitor of 40  $\mu$ F. Find out the current in the circuit, power factor, active power consumed, reactive power consumed, voltage drop across each components. [8]
- b) A circuit consisting of a resistance of  $30\Omega$  in series with an inductance of 75 mH is connected in parallel with a circuit consisting of a resistance of  $20\Omega$  in series with a capacitance of 100  $\mu$ F. If the parallel combination is connected to a 240v, 50Hz, single-phase supply, calculate (i) the current in each branch (ii) the total current and power factor, and (iii) power consumed. [8]
5. a) In the star-connected load 3 -  $\phi$  as below find neutral current when 3 -  $\phi$  supply is 415 V. [6]



- b) A load of 150 kW at 220V, 50 HZ at power factor of 0.7 lagging. Calculate the Kvar rating and capacitance of the capacitor to improve the power factor to 0.95 lagging. What will be the new supply current in this case? [6]
- c) A 3- $\phi$  500 V motor load has a power factor of 0.4. Two wattmeters connected to measure the power show the input to be 30 kw. Find the reading on each wattmeter. [4]

\*\*\*

TRIBHUVAN UNIVERSITY  
INSTITUTE OF ENGINEERING  
**Examination Control Division**


2080 Baishakh

Exam.	Back		
Level	BE	Full Marks	80
Programme	BEL, BEX, BEI, BCT, BAM, BIE, BAG, BAS, BCH	Pass Marks	32
Year / Part	I / I	Time	3 hrs.


**Subject:** - Basic Electrical Engineering (EE 401)

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

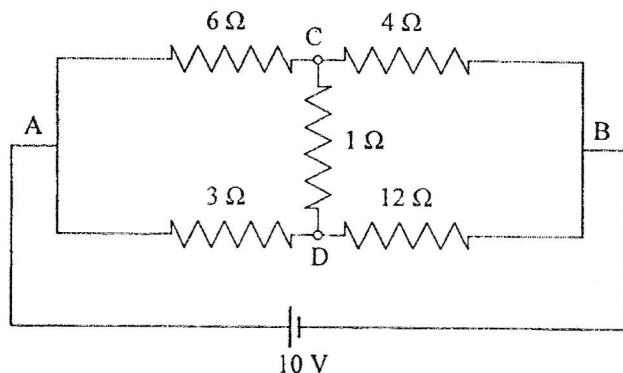1. a) The resistance of a transformer winding is  $460\ \Omega$  at room temperature of  $25^\circ\text{C}$ . When the transformer is running and the final temperature is reached, the resistance of the winding increases to  $514\ \Omega$ . Find the average temperature rise of winding, assuming that  $\alpha_{20} = 0.004/^\circ\text{C}$ . [6]
- b) What are ohmic and non ohmic conductors? Discuss voltage current characteristics of a metallic conductor. [4]
- c) In the given circuit, calculate the current flowing through  $12\ \Omega$  resistor when
  - i) C and D are open circuited.
  - ii) C and D short circuited. [6]



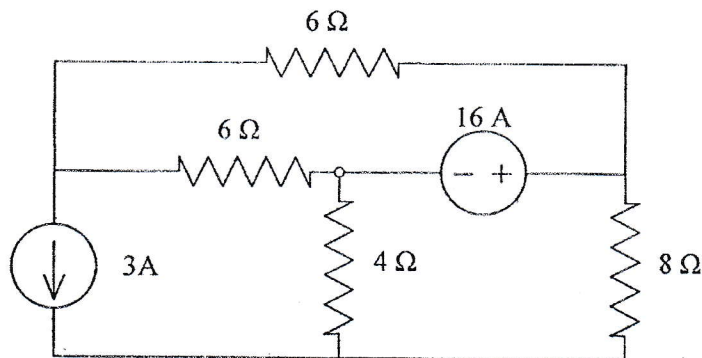
2. a) Prove that VI relation is linear but Power-voltage relation is non-linear. [4]
- b) Calculate the current through  $8\ \Omega$  resistance using Thevenin's Theorem in the given circuit. [8]






- c) Determine the value of source current in the network shown below using star delta transformation.

[4]

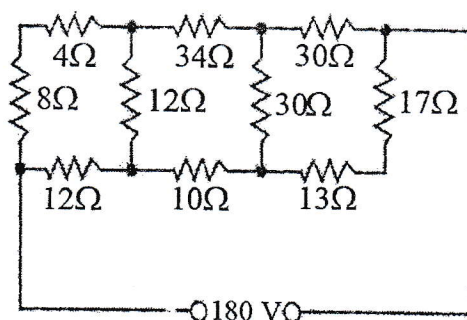

3. a) Determine the current in  $6\ \Omega$  resistor in the circuit shown below using superposition theorem.

[8]

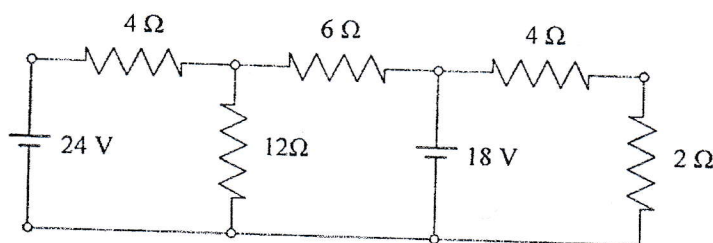


- b) Find the expression for equivalent self-inductance of two coils when they are placed near to reach to each other in parallel aiding type.
- c) Define power factor and explain cause of low power factor. Why in general, it should be kept as high as possible as in power supply systems.
4. a) Determine the average and rms value of voltage for sinusoidal voltage waveforms shown in figure below. Also find peak and form factor.

[4]

[4]

[6]

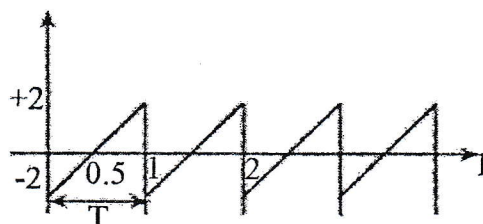

- b) Find the source current, power factor and total power consumed in the given circuit and show the main voltage and branch currents in phasor.
- c) Define the terms for an a.c quantity.
- i) Lagging (ii) Leading (ii) In phase and (iv) Out of phase be  $180^\circ$ . Draw phasor and wave diagram also.
5. a) An unbalanced star-connected load shown in figure below is supplied by three phase balanced supply of 400V, 50Hz system. Find line currents, current through neutral wire, active power, reactive power and apparent power and overall power. Also draw the phasor diagram.
- b) Write the operating principle of a wattmeter. Explain how two wattmeter can measure an active power in a 3 phase circuit.

[6]

[4]

[8]

[8]




TRIBHUVAN UNIVERSITY  
INSTITUTE OF ENGINEERING  
Examination Control Division

2080 Bhadra


Exam.	Regular		
Level	BE	Full Marks	80
Programme	BEL, BEX, BEL, BCT, BAM, BIE, BAG, BAS, BCH	Pass Marks	32
Year / Part	I / I	Time	3 hrs.

**Subject:** - Basic Electrical Engineering (EE 401)

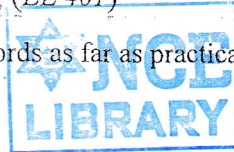
- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.



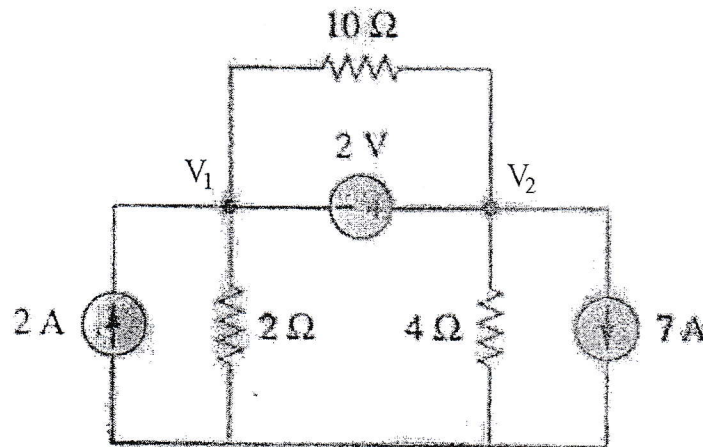1. a) Define resistance and resistivity. List out the factors affecting the resistance of a conductor. How they affect its value? [6]
- b) The field winding of dc motor takes 1.15 A current at 20°C. If current falls to 0.26 A after working for some hours, supply voltage remaining constant, find the final working temperature of field winding. Given  $\alpha_0 = \frac{1}{234.5}$  and voltage = 230V. [5]
- c) A wheatstone bridge circuit has  $R_{AB} = R_{CD} = 60\Omega$ ,  $R_{BC} = R_{AD} = 40\Omega$ ,  $R_{BD} = 100\Omega$ . Supply is connected to points A and C. If the current drawn from the supply is 100 mA, find the currents through branches  $R_{BD}$ ,  $R_{BC}$  and  $R_{DC}$ . [5]
2. a) Using Nodal method, find the current through the resistors in the circuit configuration of figure below. [6]




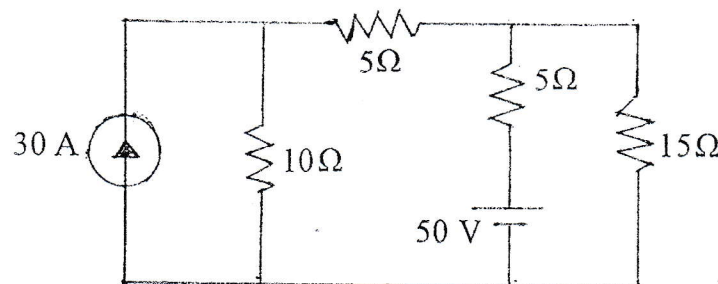- b) For the network shown in below, draw a Norton's equivalent circuit and determine the current flowing through 15Ω resistor. [6]




- c) State and verify reciprocity theorem. [4]

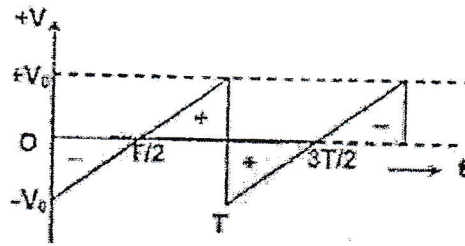3. a) Derive the equation for inductance in terms of its physical dimensions. [4]  
 b) Find (i) the average value and (ii) rms value for the Saw-tooth voltage of peak value  $V_0$  as shown in the figure below. [6]



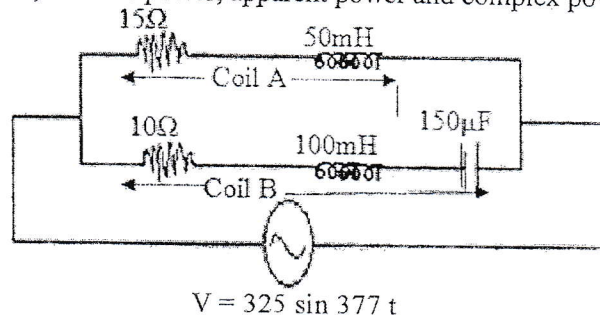- c) Derive an expression for the current drawn by a pure capacitor when connected across a sinusoidal voltage. Explain with the help of a power diagram that the value of average power drawn by the capacitor during one cycle is zero. [6]  
 4. a) A voltage  $v(t) = 254.52 \sin(377t + 10^\circ)$  is applied to a circuit. It causes a current to flow which is described by  $I(t) = 14.14 \sin(377t - 20^\circ)$ . Determine the power factor and the average power delivered to the circuit. [6]  
 b) In the network shown in figure below, calculate. [10]  
 i) Conductance, susceptance, admittance of each coil.  
 ii) Total current taken by the two coil.  
 iii) Power factor of the circuit.  
 iv) Active power, reactive power, apparent power and complex power of the circuit.



$$V = 325 \sin 377 t$$

5. a) A 400V, three phase, 50Hz induction motor takes 40 kW power from supply mains at 0.6 power factor lagging. Calculate capacitance per phase of delta (mesh) connected capacitors to improve the overall power factor to 0.95 lagging. [6]  
 b) An unbalanced three wire delta connected load has balanced voltage of 200V. The loads are  $Z_1 = 31 + j59 \Omega$ ,  $Z_2 = 30 - j40 \Omega$ ,  $Z_3 = 80 + j60 \Omega$ . Calculate [10]  
 i) Phase currents.  
 ii) Line currents.  
 iii) Active power, reactive power, apparent power and complex power

\*\*\*



TRIBHUVAN UNIVERSITY  
INSTITUTE OF ENGINEERING  
**Examination Control Division**


2079 Baishakh

Exam. Level	Back		
	BE	Full Marks	80
Programme	BEL, BEX, BEI, BCT, BAM, BIE, BAG, BAS, BCH	Pass Marks	32
	I / I	Time	3 hrs.


**Subject:** - Basic Electrical Engineering (EE 401)

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks
- ✓ Assume suitable data if necessary.

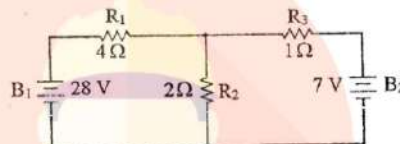
1. a) State and explain Krichof's current and voltage laws. Find the current flowing through 2 ohm resistor using KCL equations. [6]



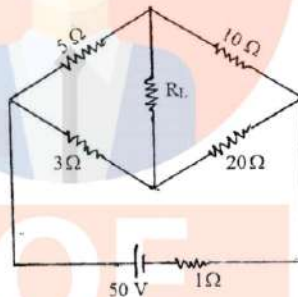- b) Find voltage across the given load resistance  $R_L$ . [10]



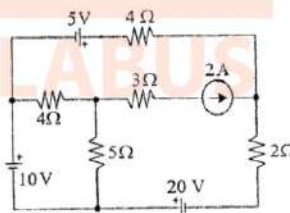2. a) Find the current supplied by 10V source using Nodal Analysis in the circuit shown in figure below. [8]



- b) State and verify Reciprocity Theorem with an example. [8]





3. a) Explain the parallel connection of inductors with suitable example and also find the equivalent inductance of the circuit. [8]  
 b) A full wave rectified sinusoidal voltage shown in figure below. Find the average and effective value of the voltage. [8]


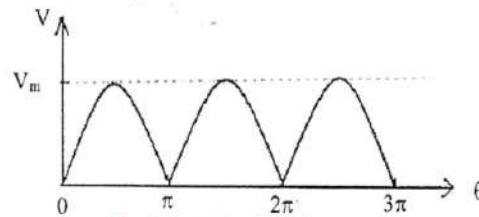


Fig: Full wave rectified sinewave

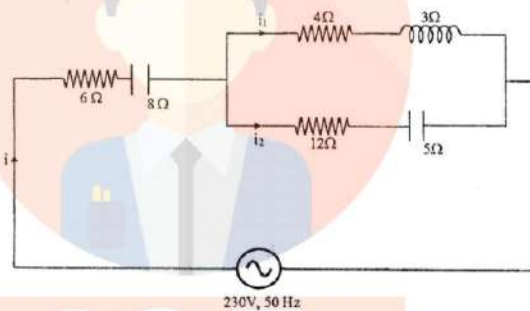4. For the circuit shown below. Calculate [16]  
 (i) Overall impedance of the circuit  
 (ii) Total current taken from supply and overall power factor of the circuit  
 (iii) Currents in each parallel branch  
 (iv) Active, reactive and apparent power  
 (v) Construct Phasor diagram for given circuit



230V, 50 Hz

5. a) Discuss the advantages of three phase system over single phase system. Mention the causes of low power factor and its measures to improve. [6]  
 b) A 380 V, 3- $\Phi$  voltage is applied to a balanced star connected 3- $\Phi$  load of phase impedance  $(5+j9)\Omega$ . If wattmeters are connected taking Y phase reference, calculate wattmeter readings and also reactive power, apparent power and active power consumed. Take RYB phase sequence. [10]

\*\*\*  
 SYLLABUS



TRIBHUVAN UNIVERSITY  
INSTITUTE OF ENGINEERING  
Examination Control Division


2078 Bhadra

Exam.	Level	Programme	Year / Part	Time
EE	4E	BEL. BEMBEL BCT. BAM. BBL ENG. BAS. ECH	I / I	3 hrs.
		Full Marks	80	
		Pass Marks	32	


Subject: - Basic Electrical Engineering (EE 401)

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

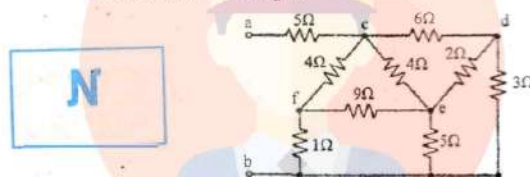
1. a) Define ideal and practical voltage source. Explain the role of internal resistance in practical voltage source with an example. [8]
- b) Using Delta-Star transformation, determine resistance between terminals a and b in the circuit shown in the figure. [8]



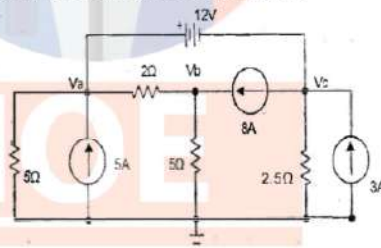2. a) Find the current through  $2\Omega$  resistor using mesh analysis. [8]




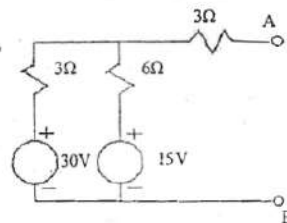- b) Find the value of resistance to be connected across the terminals A and B to transfer maximum power to it and find the value of this maximum power for the network shown below. [8]






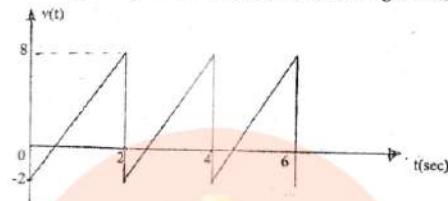3. a) Calculate the average value, rms value and form factor of the given voltage signal. [8]



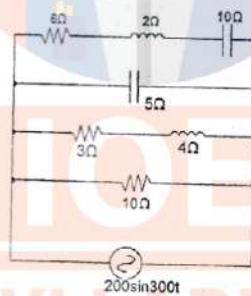- b) A single phase inductive load of 4kW at a power factor of 70% (lagging) is connected across 240V, 50Hz supply. Calculate the kVAR capacity of the capacitor bank and value of capacitance that must be installed in parallel with load to bring the overall power factor to (i) unity, (ii) 85% lagging. [8]
4. In the network shown in figure below, determine: [16]
- Total impedance
  - Total current drawn from source
  - The overall power factor
  - Total Volt Amperes, Active Power and Reactive Power
  - Is the circuit capacitive or inductive?
  - Construct the phasor diagram for given circuit.



5. a) The star-connected load having impedance of  $(12-j16)\Omega$  per phase fed from a 50Hz three-phase, 400V, balanced supply, with the phase sequence as R-Y-B. Find the line current, power factor, active power, reactive power, reactive VA and total volt-amperes (VA). [10]
- b) Describe the measurement of 3-phase power by two wattmeter method. [6]

\*\*\*





TRIBHUVAN UNIVERSITY  
INSTITUTE OF ENGINEERING  
Examination Control Division


2078 Kartik

Exam.	Back		
Level	BE	Full Marks	80
Programme	BEL, BEX, BEI, BCT, BAM, BIE, BAG, BAS, BCH	Pass Marks	32
Year / Part	1 / 1	Time	3 hrs.


**Subject: - Basic Electrical Engineering (EE 401)**

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

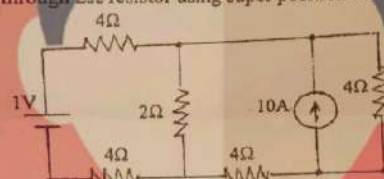
1. a) At  $20^{\circ}\text{C}$ , two coils connected in series having resistance of  $600\Omega$  and  $300\Omega$  respectively. The temperature coefficient at  $20^{\circ}\text{C}$  are  $0.002/^{\circ}\text{C}$  and  $0.004/^{\circ}\text{C}$  respectively for the coils. Find the resistance of combination at a temperature of  $50^{\circ}\text{C}$ . What is the effective temperature co-efficient of the combination at  $50^{\circ}\text{C}$ ? [8]
- b) Find the current through  $2\Omega$  resistor using super position theorem in the circuit below. [8]



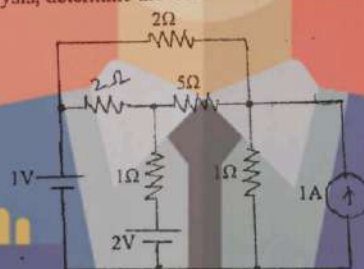2. a) Using Nodal Analysis, determine the current in  $5\Omega$  resistor in the circuit below. [8]




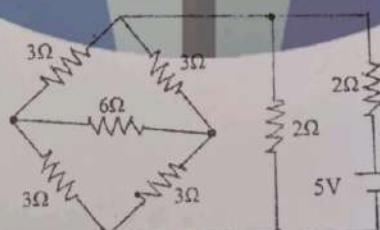- b) State Thevenin's theorem. Determine the current through  $6\Omega$  resistor using Thevenin's theorem. [8]






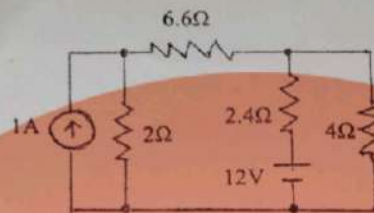3. a) Use Norton's theorem to calculate the current through  $4\Omega$  resistance in the circuit below. [8]



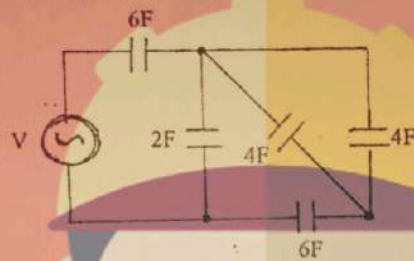- b) Calculate the equivalent capacitance in the circuit shown below. [4]



- c) What are the drawbacks of low power factor? Explain a measure to improve power factor. [4]
4. a) Determine the rms and average value of the given waveform. [8]



- b) Two circuits the impedances of which are given by  $Z_1 = (10 + j15)$  and  $Z_2 = (6 - j8)$  are connected in parallel. If the applied voltage to the combination is 230V, find (i) current and pf of each branch (ii) overall current and p.f. of the combination (iii) power consumed by each impedance and (iv) Draw the phasor diagram. [8]
5. a) Derive an expression to calculate the power factor of load (lagging) using two wattmeter meter readings. Also, explain the effect of power factor on wattmeter readings. [4+4]
- b) Three loads  $3 + j5$ ,  $3 - j4$  and  $8 + j6$  are connected in delta to a 3-phase, 400V supply. Find the phase currents, line currents and total power consumed. [8]

\*\*\*

TRIBHUVAN UNIVERSITY  
INSTITUTE OF ENGINEERING  
**Examination Control Division**


2076 Chaitra

Exam.	Regular		
Level	BE	Full Marks	80
Programme	BEL, BEX, BEI, BCT, BAM, BIE, BAG, BAS, BCH	Pass Marks	32
Year / Part	I / I	Time	3 hrs.


**Subject:** - Basic Electrical Engineering (EE 401)

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

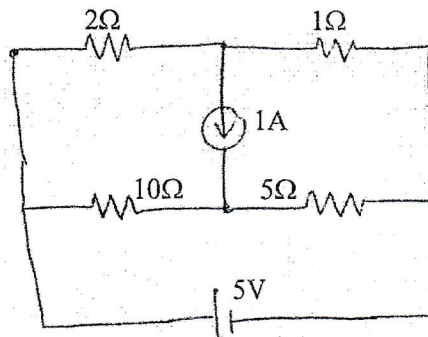
1. a) What do you mean by ideal and practical voltage source? Explain the effect of an internal resistance of voltage and current sources on their terminal characteristics. [4+4]
- b) Using loop current method, determine the current through  $5\Omega$  resistor in the circuit below. [8]



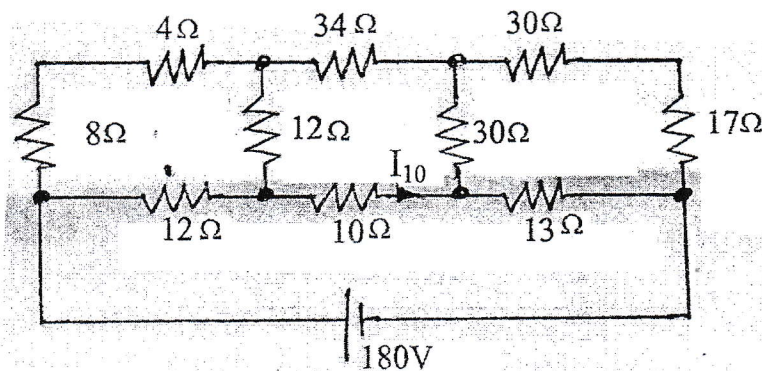2. a) Find the  $I_{10}$  using Y/ $\Delta$  transformation method, in the network given below. [8]




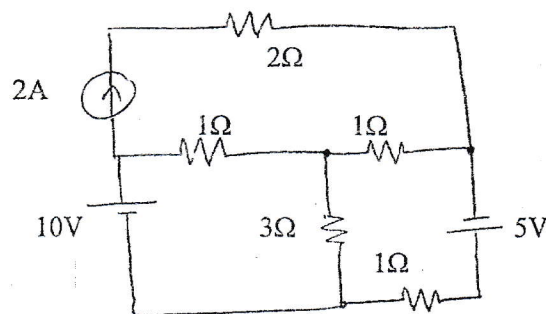- b) Find the current through  $3\Omega$  resistor using Thevenin's theorem. [8]






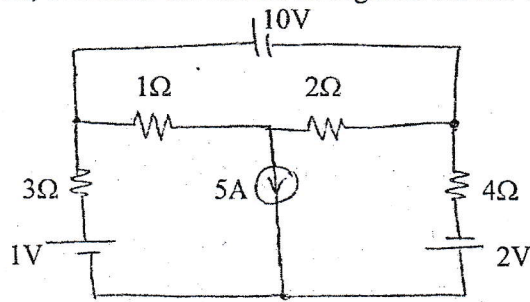3. a) Using Nodal analysis, determine the current through  $2\Omega$  resistor in the circuit below. [8]



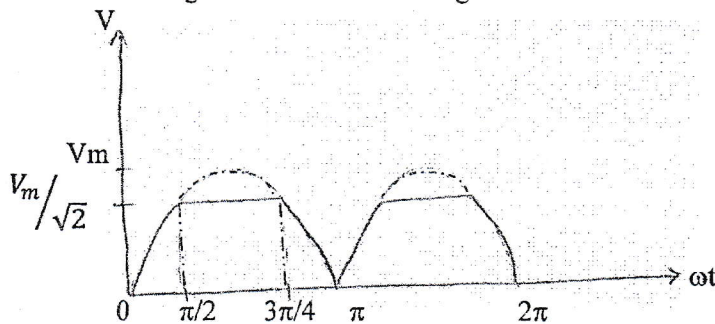- b) What is a self inductance? Derive the expression of equivalent inductance, when the two inductances are connected in series (opposing). [4]  
 c) "The average power over complete cycle in a purely inductive circuit is zero". Justify with necessary waveforms and mathematical expression. [4]
4. a) Find the rms and average value of the following waveform. [8]



- b) Two coils A & B are connected in series across a 230V, 50Hz ac supply. The resistance and inductance of coil A & B are  $5\Omega$  and 0.018H respectively. The input from the supply is 2KW and 2kVAR, find the inductance of coil A and resistance of coil B. Also calculate the voltage across each coil. [8]
5. a) A two wattmeters measured an input power of 30KW and 40KW respectively to a motor. If the power factor of the motor be changed to 0.85 leading, determine the two wattmeter readings. The total input power remains the same. Draw a phasor diagram for the second condition. [8]
- b) Three loads  $4-3j$ ,  $6+8j$ , and  $8+6j$  are connected in delta to a 3-phase, 400V supply. Find phase currents, line currents and total power consumed. [8]

\*\*\*


TRIBHUVAN UNIVERSITY  
INSTITUTE OF ENGINEERING  
**Examination Control Division**  
2076 Ashwin

Exam.	Back		
Level	BE	Full Marks	80
Programme	BEL, BEX, BEI, BCT, BAM, BIE, BAG, BAS	Pass Marks	32
Year / Part	I / I	Time	3 hrs.


**Subject: - Basic Electrical Engineering (EE 401)**

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

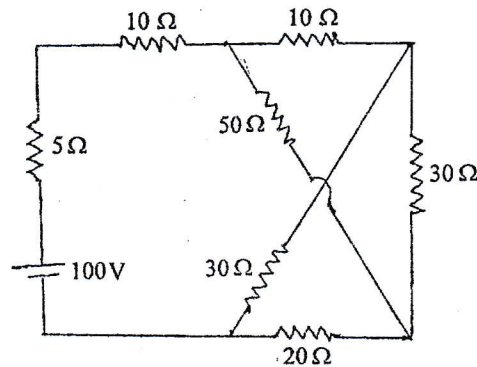
1. a) What are ideal and practical voltage and current source? Explain. [4]
- b) A coil has a resistance of  $18\ \Omega$  when its mean temperature is  $20^\circ\text{C}$  and of  $20\ \Omega$  when its mean temperature is  $50^\circ\text{C}$ . Find its mean temperature rise when its resistance is  $21\ \Omega$  and the surrounding temperature is  $15^\circ\text{C}$ . [6]
- c) State and explain Kirchoff's voltage laws. Determine the current supplied by the battery in the circuit shown in figure below. [6]



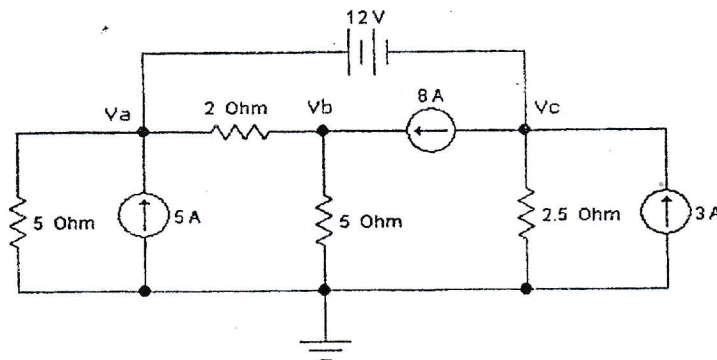
2. a) Use Nodal Analysis Method to determine the  $V_a$ ,  $V_b$  and  $V_c$  and Calculate current through  $2\ \Omega$ . [8]



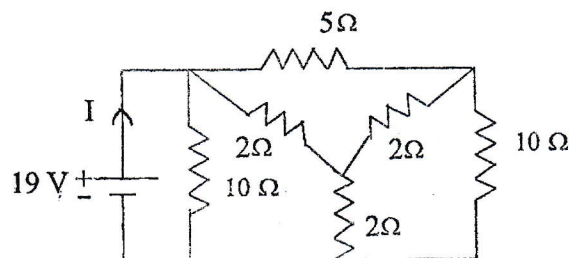
- b) Find the current  $I$  as shown in figure using star – delta transformation. [8]



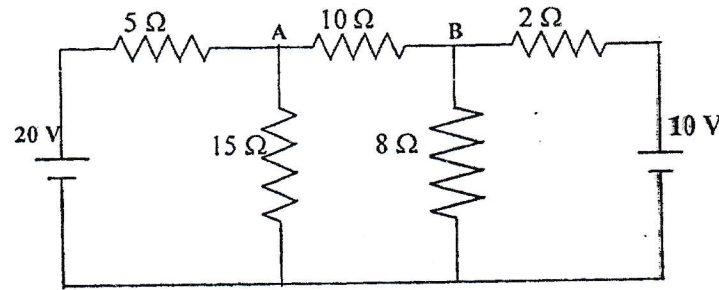3. a) Calculate the current in the  $10\Omega$  resistor in the networks shown in the circuit using Thevenin's Theorem. [8]



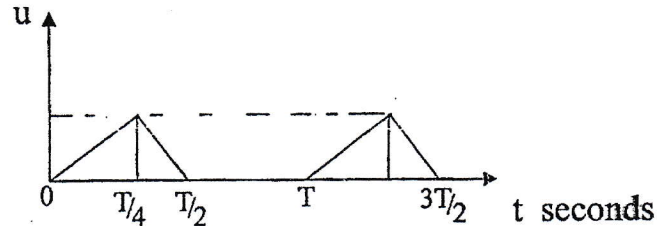- b) Explain what is mean by self inductance and mutual inductance of a coil. [4]  
 c) Calculate the average and rms value of the waveform shown below, over one cycle. [4]



4. a) State and explain reciprocity theorem with a suitable example. [4]  
 b) A resistance of  $20\Omega$ , an inductance of  $0.2\text{ H}$  and a capacitance of  $100\text{ }\mu\text{F}$  are connected in series across a  $220\text{ V}$ ,  $50\text{ Hz}$  supply. Determine the following (i) impedance (ii) current (iii) voltage across R, L and C. [4]  
 c) Two impedances  $z_1$  and  $z_2$  are connected in parallel. The first branch takes a leading current of  $16\text{ A}$  and has a resistance of  $5\Omega$ , while the second branch takes a lagging current at power factor  $0.8$ . The total power supplied is  $5\text{ kW}$ , the applied voltage being  $(100+j200)\text{ V}$ . Determine the branch and total currents. [8]  
 5. a) What are the disadvantages of supplying a low power factor? A  $100\text{ KW}$  load at  $0.85$  lagging power factor is being supplied by a  $230\text{ V}$ ,  $50\text{ Hz}$  source. Calculate the reactive power drawn from the source. If a capacitor connected parallel to the load improves its power factor to  $0.9$ , find the capacitance of the capacitor. Also, calculate the current drawn from the source before and after connecting the capacitor. [2+6]  
 b) A three phase delta connected system with  $400\text{ V}$  line voltage is connected to three unbalanced loads:  $(12-j16)\Omega$ ,  $(3+j4)$ , and  $20\Omega$ , are also connected in delta. Find (i) phase currents (ii) line currents (iii) total active power consumed. [8]

\*\*\*




Exam.	Regular / Back		
Level	BE	Full Marks	80
Programme	BEL, BEX, BEI, BCT, BAM, BIE, BAG, BAS	Pass Marks	32
Year / Part	I / I	Time	3 hrs.


**Subject: - Basic Electrical Engineering (EE 401)**

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

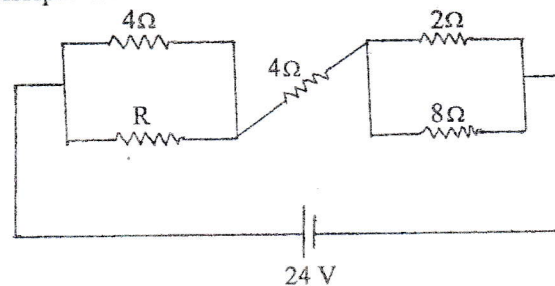
1. a) Discuss on brief voltage and current sources. Also justify the statement "terminal voltage goes on increasing on decreasing load current". [4]
- b) The resistance of the certain length of wire is 4.60 ohm at 20°C and 5.68 ohm at 80°C. Determine (i) the temperature coefficient of resistance of the wire at 0°C, (ii) the resistance of the wire at 60°C. [6]
- c) State and explain Kirchoff's current laws. Determine the value of unknown resistance R and the total current drawn from the source in the circuit of figure. Also compute the total power dissipated in the circuit. [6]



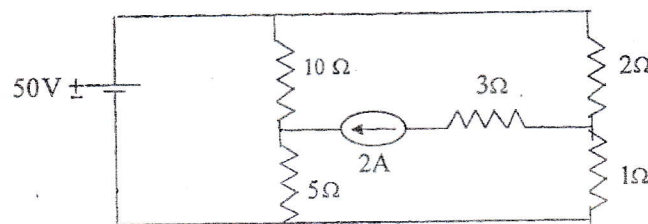2. a) Use loop current method to calculate the current through the 5 Ω resistance for the network shown below. [8]




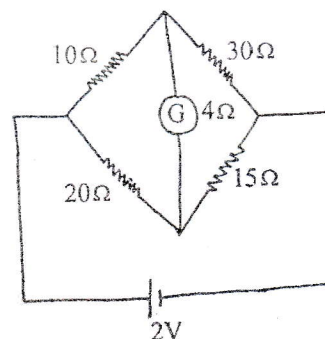- b) Using delta/star transformation, find the galvanometer current in the Wheatstone bridge. [8]



3. a) Find the current through R using thevenin's theorem. Also, find the value of R such that maximum power transfer takes place from the source to R in the network shown below.


[8]

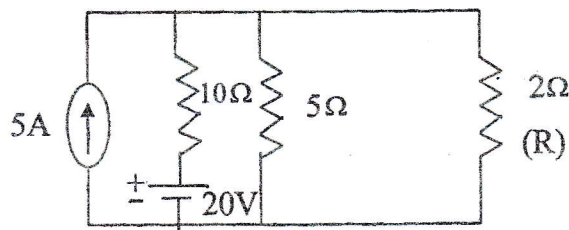

- b) Derive an expression for the equivalent capacitance of a group of capacitors when they are connected in series.
- c) Calculate the form factor and peak factor of the following waveform.

[4]

[4]

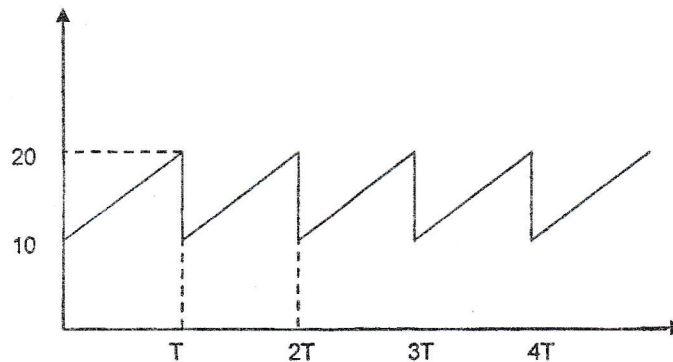

4. a) State and explain Norton's theorem with a suitable example.
- b) A resistance of  $12\ \Omega$ , an inductance of  $0.15\ \text{H}$  and a capacitance of  $130\ \mu\text{F}$  are connected in series across a  $100\text{V}$ ,  $50\text{Hz}$  supply. Calculate the impedance, current and phase angle and power factor.
- c) A parallel circuit consists of two branches, one containing a coil of resistances  $5\ \Omega$  and inductance  $38.2\text{mH}$ , the other a non-inductive resistance  $16\ \Omega$  in series with a capacitor of  $300\ \mu\text{F}$  capacitance. The circuit is connected to a  $240\ \text{V}$ ,  $50\ \text{Hz}$  supply. Determine (i) the current in each branch (ii) the total current (iii) the circuit phase angle (iv) the circuit impedance (e) the components of an equivalent circuit consisting of a resistance and reactance.
5. a) Define power factor and explain causes of low factor. A single phase  $240\text{V}$ ,  $50\ \text{Hz}$  induction motor takes  $20\text{A}$  at power factor of  $0.75$  lagging. It is desired to raise the power factor to  $0.95$  lagging by connecting a capacitor across the load. Calculate the capacitance of the capacitor to be used in parallel with induction motor.
- b) A three phase  $400\ \text{V}$ ,  $50\ \text{Hz}$  power line has two loads connected to it. The first is delta-connected and draws  $25\ \text{Kw}$  at  $0.70$  power factor lagging. The second is wye-connected and draws  $6.25\ \text{kVA}$  at  $0.8$  power factor leading. What is the total line current and the combined power factor.

[4]

[4]

[8]

[2+6]

[8]

\*\*\*




Exam.	Back		
Level	BE	Full Marks	80
Programme	BEL, BEX, BCT, BAME, BIE, B. Agri.	Pass Marks	32
Year / Part	I / I	Time	3 hrs.


**Subject: - Basic Electrical Engineering (EE401)**

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

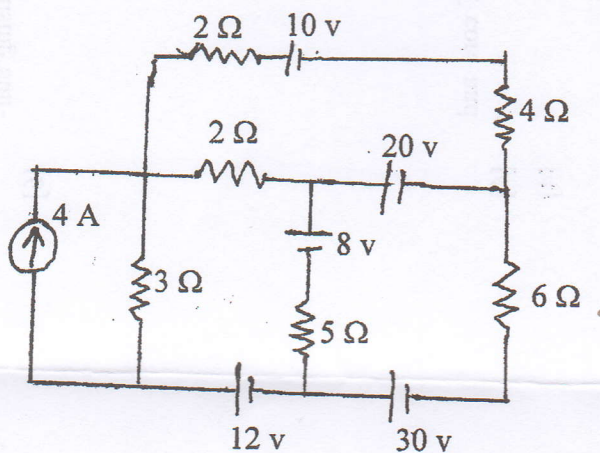1. a) Differentiate between Practical Voltage Source and Practical Current Source. [4]
- b) The field winding of dc motor takes 1.15 A current at 20°C. If current falls to 0.26 A after working for some hours, supply voltage remaining constant, find the final working temperature of field winding. Given,  $\alpha_0 = \frac{1}{234.5}$  and voltage = 230V. [6]
- c) Three lamps of rating 220 V and 150 watt, 200 watt and 450 watt are connected across 200 V supply. Calculate the resistance of each lamp and the power consumed by each lamp at 200 V. [6]
2. a) Solve the given network with mesh analysis to find voltage drop on 5  $\Omega$  resistors. [6]



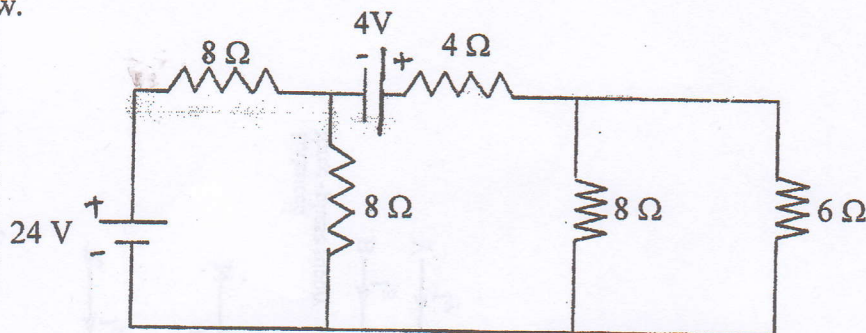- b) Use nodal analysis to find the current through 4 $\Omega$  resistor for the network shown below. [6]




- c) State and explain superposition theorem with suitable example. [4]




3. a) Using thevenin's theorem find the current through the  $4\Omega$  for the network shown below.

[6]

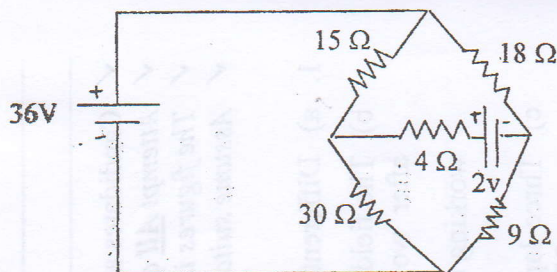

- b) Determine the power dissipated in the  $8\Omega$  resistor of the given network using star-delta and delta-star transformation.

[6]

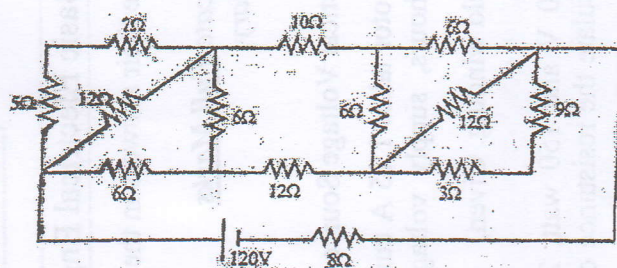


- c) How mutual inductance between two coils depends upon dimensions of core and coils.

[4]

4. a) Find the form factor and peak factor of the current waveform given below.

[4]

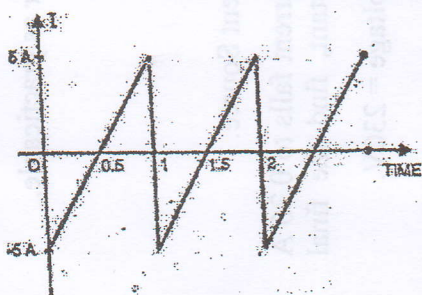

- b) A coil of inductance  $318.3 \text{ mH}$  is connected in series with a  $200\Omega$  resistor to a  $240 \text{ V}$ ,  $50 \text{ Hz}$  supply. Calculate the current flowing, power factor, active and reactive power of the circuit. Also draw the phasor diagram.


[6]

- c)  $Z_1 = (40 - j318.31)$  and  $Z_2 = (50 + j62.83)$  are connected in parallel to each other and a source of  $100 \text{ V}$ ,  $50 \text{ Hz}$  is applied across the overall circuit. Calculate (i) circuit current (ii) Active, reactive and apparent power.

[6]



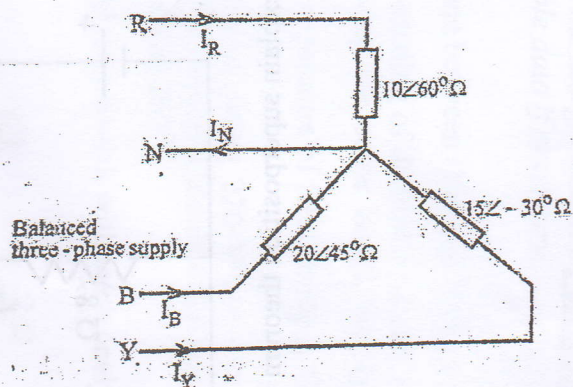5. a) Discuss the effect of low power factor. A single phase load of 7Kw operates at a power factor 0.7 lagging. It is proposed to improve the power factor to 0.9 lagging by connecting a capacitor the load. Calculate the KVAR rating of the capacitor. [3+5]
- b) For the following unbalanced system with balanced three phase supply of 400 V, 50 Hz, calculate: [8]
- The line currents and neutral current
  - Active and reactive power absorbed by the circuit
  - Draw the phasor diagram.




\*\*\*

Exam.	Back	
Level	BE	Full Marks 80.
Programme	BEL, BEX, BAME, BCT, BIE, B.Agric.	Pass Marks 32
Year / Part	I / I	Time 3 hrs.


**Subject:** - Basic Electrical Engineering (EE401)

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

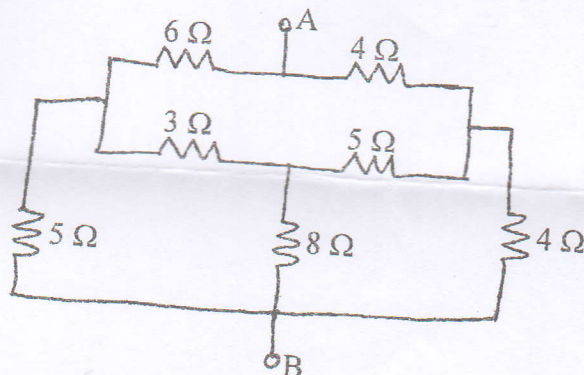1. a) What do you mean by ideal and practical voltage and current source? Explain the method for converting practical voltage source into current source and vice versa. [5]
- b) A 60 watt, 240 V incandescent filament lamp is switched on at 20°C. The operating temperature of the filament is 2000°C. Determine the current taken by the lamp at the instant of switching ON. The temperature coefficient of resistance of the filament material is 0.0045°/k. [6]
- c) A circuit containing three resistors with resistances 12Ω, 18Ω and 36Ω respectively joined in parallel is connected in series with a fourth resistance. The whole circuit is supplied at 60V and it is found that power dissipated in 12Ω resistance is 36watt. Determine the value of fourth resistance and the total power dissipated in the group. [5]
2. a) Make comparison table between series and parallel circuit. [4]
- b) For the circuit shown in below figure, determine the resistance between points A and B using star / delta transformation theorem. [6]



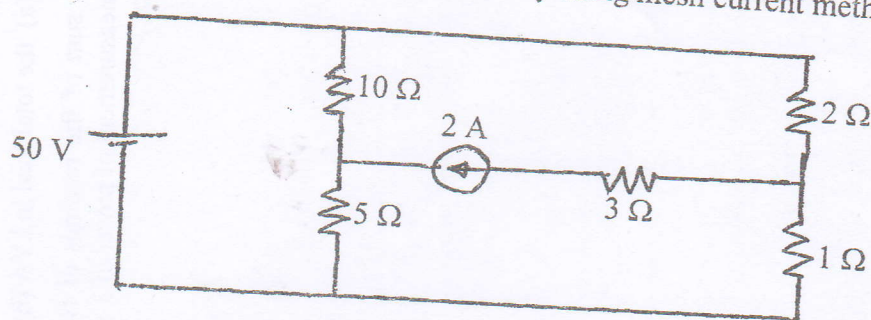
- c) Find all branch currents in the given circuit by using mesh current method. [6]






3. a) Using Nodal analysis, determine currents in each branch of the network shown in below figure. Also find the total power loss in the network.

[8]

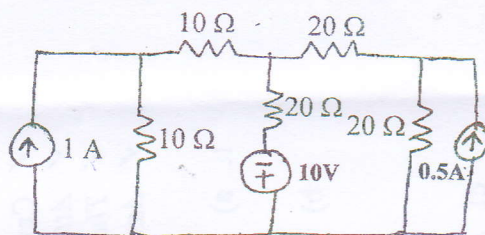

- b) Find the value of Resistance 'R' to have maximum power transfer in the circuit as shown in below figure. Also obtain the amount of maximum power.

[8]

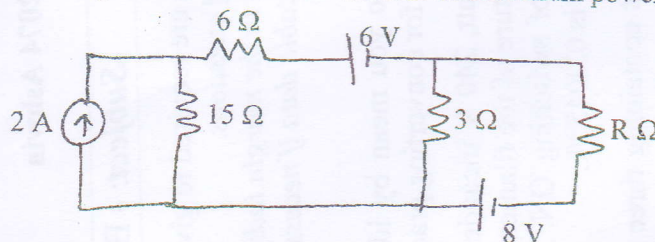

4. a) Two inductances  $L_1$  and  $L_2$  are connected in parallel. Derive the relation showing the equivalent inductance of the combination when mutual flux helps the individual flux. what will be the equivalent inductance of the combination when mutual flux opposes the individual flux?

[4]

- b) Two alternating currents represented by the equations  $i_1 = 7\sin\omega t$  and  $i_2 = 10\sin\left(\omega t + \frac{\pi}{2}\right)$  are fed into a common conductor. Find the equation for the resultant current and its RMS value.


[4]

- c) Below Figure shows a series parallel circuit. Find:

[8]

- total impedance
- current drawn from the circuit
- voltage across the parallel branches
- current flowing through each parallel branch
- power factor
- Active, reactive and apparent power

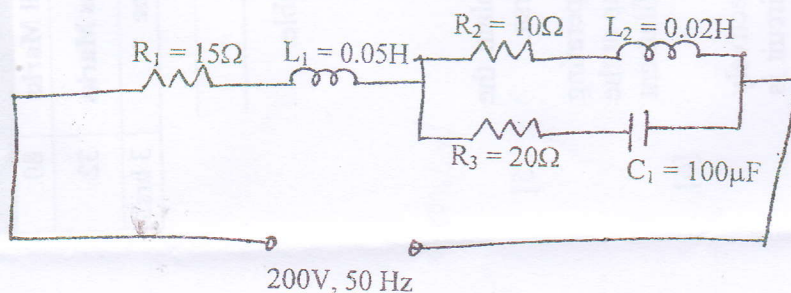Also, draw the phasor diagram of the circuit.



5. a) A fluorescent lamp takes a current of 0.75A when connected across a 240V, 50Hz a.c supply. The power consumed by the lamp is 80 watt. Calculate the value of the capacitance to be connected in parallel with the lamp to improve the power factor to (i) unity (ii) 0.95 lagging. [6]

b) The following balanced three phase loads are connected to a 415 V, three phase, four wire supply. [4]

(i) 160 kVA at 0.7 power factor lagging

(ii) 50 kVA at 0.65 power factor leading

(iii) 50 kW at unity power factor

Calculate (a) the total load in kVA (b) the line current (c) the combined power factor

c) Prove that sum of the readings of two wattmeters is equal to the total three phase power in measurement of power of 3-phase circuit by 2 wattmeter method. [6]

\*\*\*




Exam.	Regular		
Level	BE	Full Marks	80
Programme	BEL, BEX, BCT, BAME, BIE, B. Agri.	Pass Marks	32
Year / Part	I / I	Time	3 hrs.


**Subject:** - Basic Electrical Engineering (EE401)

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

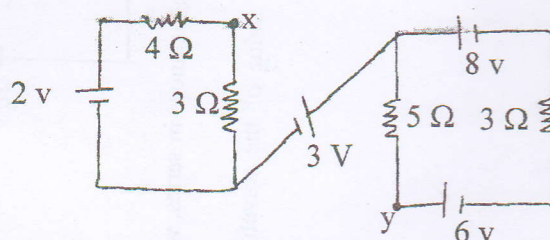
1. a) What is source transformation? Explain with the help of an example. [4]
- b) A coil of stranded copper wire having a resistance of  $12\Omega$  at  $25^\circ\text{C}$  is embedded in the core of a large transformer supplied at 230 V. After the transformer has been in service for several hours, the resistance of the coil is found to be  $13.4\Omega$ . What is the temperature of the core? Also find the power rating of the resistance. Assume temperature coefficient of wire as  $0.00125/^\circ\text{C}$  at  $15^\circ\text{C}$ . [6]
- c) Find  $V_{xy}$  in the following circuit diagram. [6]



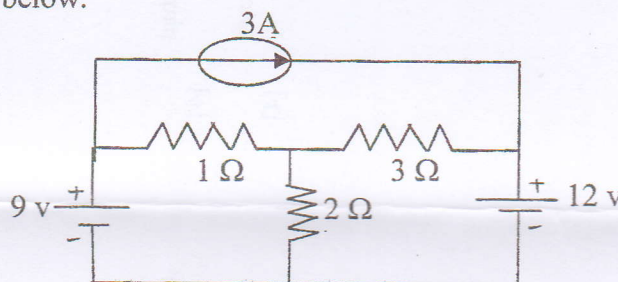2. a) Use loop current method to calculate the current through the  $2\Omega$  resistance for the network shown below. [6]



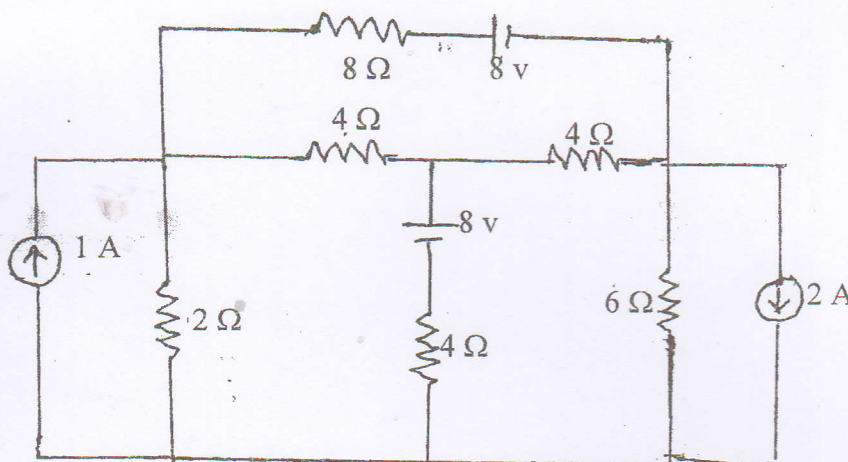
- b) Solve the given network with nodal analysis to find voltage drop on  $8\Omega$  resistor. [6]



- c) State and explain Norton's theorem with suitable example. [4]


3. a) Find power dissipated in  $3\ \Omega$  resistor using Norton's theorem.

[6]

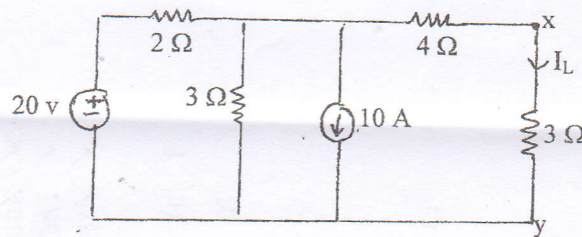

- b) Calculate the value of 'R' such that maximum power will be absorbed by it in the given circuit.

[6]

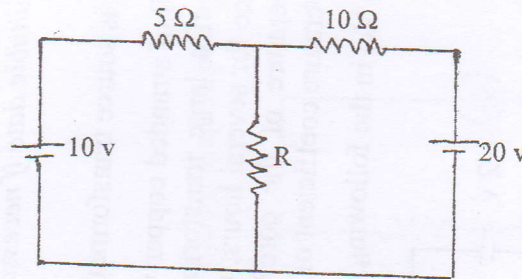


- c) What is inductance? Derive the expression for two inductances in series, with mutual flux aiding each other.

[4]

4. a) Calculate the average (half period) value and rms value of the waveform shown below.

[4]

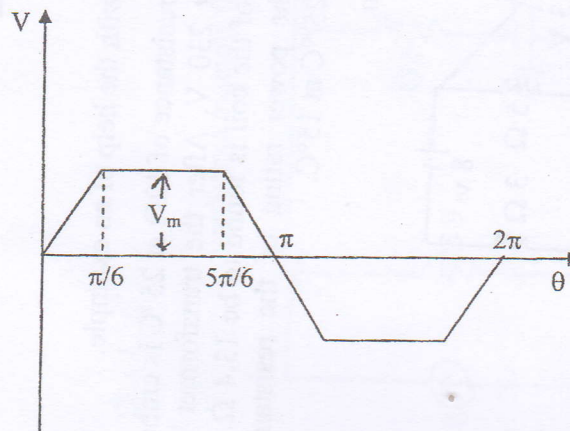


- b) An alternating source of emf  $v = 200\sin(314t)$  volts is applied to a practical coil with resistance  $20\ \Omega$  and inductance  $0.1\ \text{H}$  respectively. Determine (i) expression for instantaneous current and power factor (ii) active reactive and apparent power of circuit (iii) voltage drop on resistor and inductor and (iv) construct phasor diagram for above circuit.

[6]

- c) Find current flowing in each branches of the following circuit:

[6]

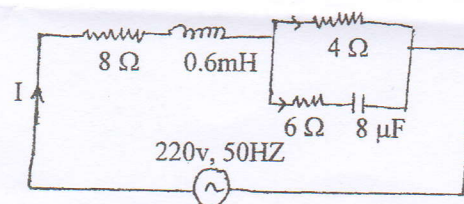



5. a) A 400V, 50 HZ, 3 phase induction motor takes 60 KW power from supply mains at 0.8 power factor lagging. Calculate the capacitance per phase and KVAR rating per phase of capacitor in order to improve the power factor to 0.9 lagging using (i) star connected capacitor bank and (ii) Delta connected capacitor bank. [8]
- b) Define phase order and explain its significance. A three phase balanced star connected load with  $(6+j8)$  ohm per phase is supplied by 400V, 50 HZ three phase source. Find the line and phase currents and the total power dissipated in the load. [2+6]

\*\*\*


2073 Shrawan

Exam.	New Back (2066 & Later Batch)		
Level	BE	Full Marks	80
Programme	BEL, BEX, BCT, BAME, BIE, B. Agri.	Pass Marks	32
Year / Part	I / I	Time	3 hrs.


**Subject:** - Basic Electrical Engineering (EE401)

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

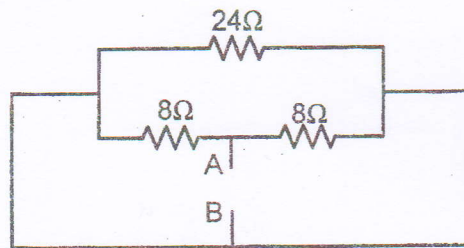
1. a) A coil has a resistance of 100 ohms, when the temperature is 20°C and 110 ohms when the temperature is 45° C. Find temperature rise when its resistance is 124 ohms, and surrounding temperature is 15° C. [6]
- b) Find the equivalent resistance between A and B for the network shown in figure below. [4]



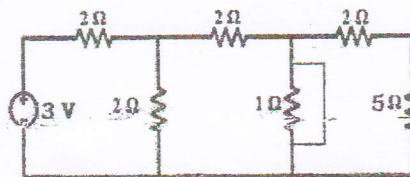
- c) Find current from the source in the following circuit diagram. [6]



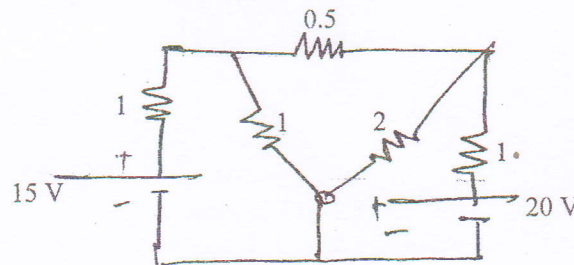2. a) Find the current in 5-ohm resistor in the network shown below by using superposition theorem. [8]




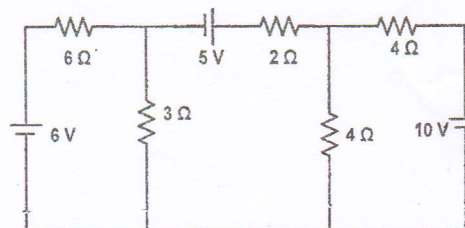- b) Find the branch currents in the circuit of figure below by using nodal analysis. [8]






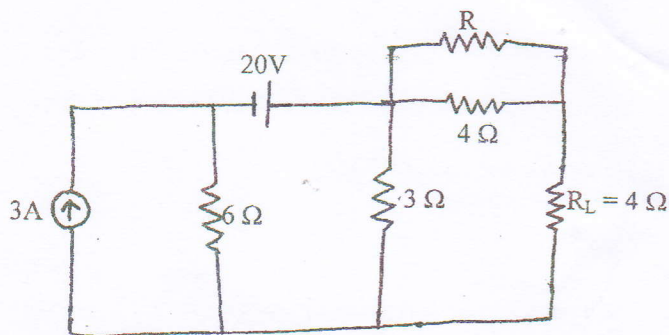
3. a) Find the value of Resistance 'R' such that the load resistance ' $R_L$ ' which is equal to  $4\ \Omega$ , will deliver maximum power. Also find that maximum power. [8]



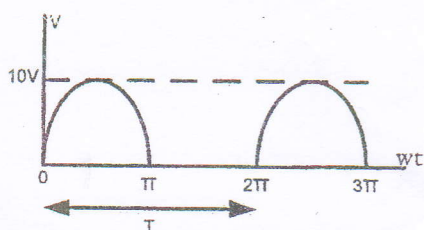- b) Derive an equation for inductance L in terms of flux linkages and current change. [4]  
 c) Calculate the (i) average value and (ii) RMS value of voltage wave shown in figure below: [4]



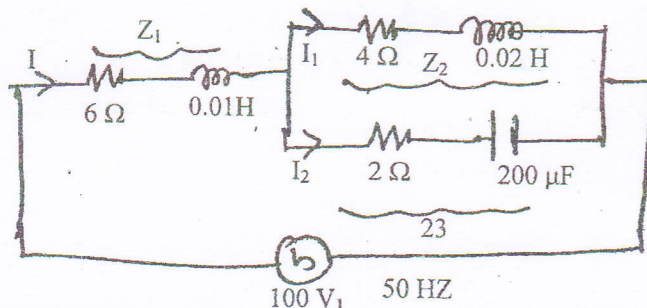4. a) Determine the value of current  $I_1$ ,  $I_2$  and  $I$  and overall factor of the circuit shown in figure below for series and parallel circuit. Also draw the phasor diagram and find the total power consumed by the circuit. [8]



- b) A coil is connected in series with a non-inductive resistance of  $30\ \Omega$  across  $240\text{V}$ ,  $50\text{Hz}$ ,  $1\text{-}\phi$  supply. The reading of voltmeters across the coil is  $180\text{V}$  and across the resistance is  $130\text{V}$ . Calculate, [8]  
 i) Inductance of coil  
 ii) Resistance of coil  
 iii) Power absorbed by coil  
 iv) Power absorbed by whole circuit
5. a) Define power factor and explain why in general it should be kept on high as possible in power supply system. [8]  
 b) Three similar coils each of resistance  $7\ \Omega$  and inductance of  $0.03\text{H}$  are connected in Delta to a  $400\text{V}$ ,  $3\text{ phase}$ ,  $50\text{Hz}$  supply. Calculate the line current and the total power consumed. [8]


Exam.	Regular		
Level	BE	Full Marks	80
Programme	BEL, BEX, BCT, BAME, BIE, B.Agric.	Pass Marks	32
Year / Part	1 / I	Time	3 hrs.

**Subject:** - Basic Electrical Engineering (EE401)


- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

1. a) A 60 W, 240 V incandescent filament lamp is switched on at 20°C. The operating temperature of the filament is 2000°C. Determine the current taken by the lamp at the instant of switching ON. the temperature coefficient of resistance of the filament material is 0.0045/K. [6]

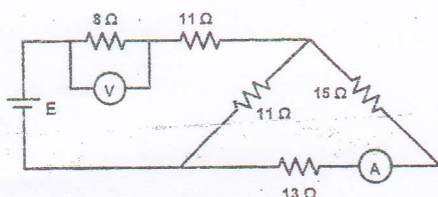
- b) A battery of unknown emf is connected across resistances, as shown in figure below. The voltage drops across the 8 Ω resistor is 20 V. What will be the current reading in the ammeter? What is the emf of the battery? [5]



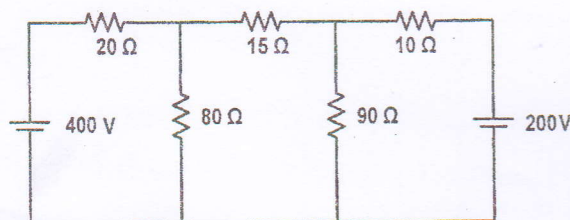- c) What do you mean by ideal and practical voltage and current sources? [5]
2. a) Find the power dissipation in 15 Ω resistor shown in figure below using mesh analysis. [6]



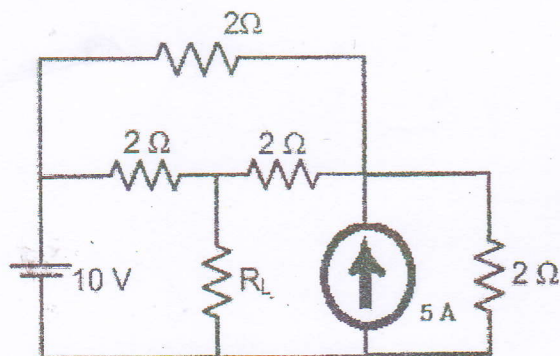- b) Find current on load resistor  $R_L$ , if its resistance is 2 Ω, using superposition theorem. [6]




- c) State and explain Norton's theorem with an appropriate example. [4]



3. a) Find the value of  $R_L$  for which the maximum power is transferred in the load resistance  $R_L$ . Also find the maximum power that can be transferred to the load resistance  $R_L$ .

[8]

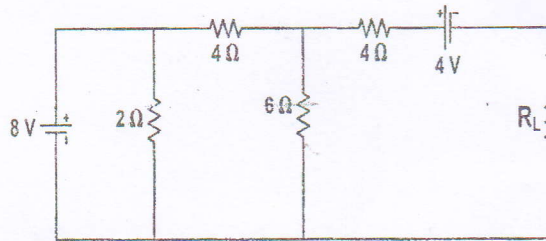


- b) Derive the expression for the inductance of inductor in terms of its physical dimensions.

[4]

- c) Calculate the average and rms value of full-wave rectified sine wave as shown below.

[4]

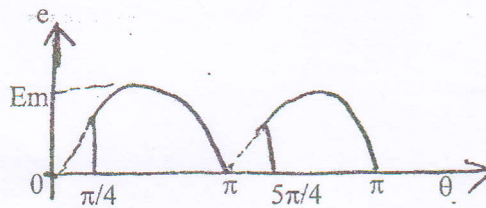

4. a) A circuit consisting of a resistance of  $30\ \Omega$  in series with an inductance of  $75\text{ mH}$  is connected in parallel with a circuit consisting of a resistance of  $20\ \Omega$  in series with a capacitance of  $100\ \mu\text{F}$ . If the parallel combination is connected to a  $240\text{ V}$ ,  $50\text{ Hz}$  single phase supply, calculate (i) The current in each branch (ii) The total current and power factor and (iii) Power consumed. Also draw a neat phasor diagram.

[8]

- b) For a series path with a resistance of  $8\ \Omega$ , capacitor of  $120\ \mu\text{F}$  and an inductance of  $0.1\text{ H}$ , a capacitor  $180\ \mu\text{F}$  is kept in parallel. Then the combination is fed by  $240\text{ V}$ ,  $50\text{ Hz}$ ,  $1\text{-}\phi$  supply. Calculate branch currents, total current from supply, power factor of whole circuit, active power and reactive power consumed by the circuit. Also show phasor diagram.


[8]

5. a) Develop relation between phase voltage and line voltage in  $3\text{-}\phi$  star connected system.

[4]

- b) For the circuit shown in figure below, calculate the current through the neutral and the total power consumed in the load.

[8]

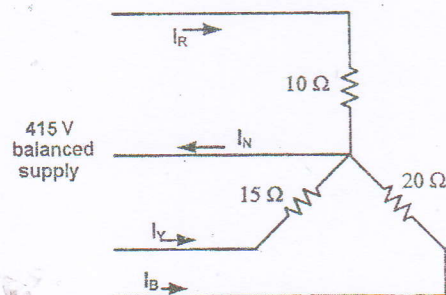

- c) Explain with connection diagram the measurement of  $3\text{-}\phi$  power using two wattmeters.

[4]


\*\*\*

Exam.	New Back (2066 & Later Batch)		
Level	BE	Full Marks	80
Programme	BEL, BEX, BCT, BIE, B.Agric.	Pass Marks	32
Year / Part	I / I	Time	3 hrs.


**Subject: - Basic Electrical Engineering (EE401)**

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

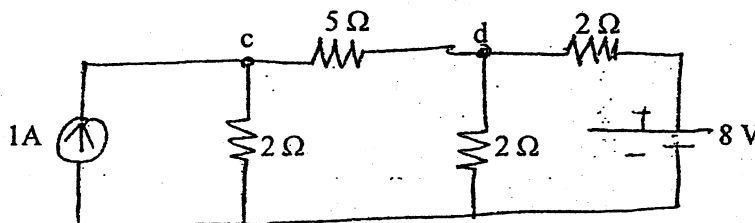
1. a) Explain ideal current and voltage sources. [4]
- b) Define temperature coefficient of resistance. The resistance of a certain length of wire is  $4.6\Omega$  at  $20^\circ\text{C}$  and  $5.88\Omega$  at  $80^\circ\text{C}$ . Determine (a) The temperature coefficient of resistance of the wire at  $0^\circ$  (b) The resistance of the wire at  $60^\circ\text{C}$ . [8]
- c) State and explain Superposition theorem with an appropriate example. [4]
2. a) Find out the current through  $5\text{ ohm}$  resistor connected across the terminal c and d in the network shown below using the Venin's theorem. [8]



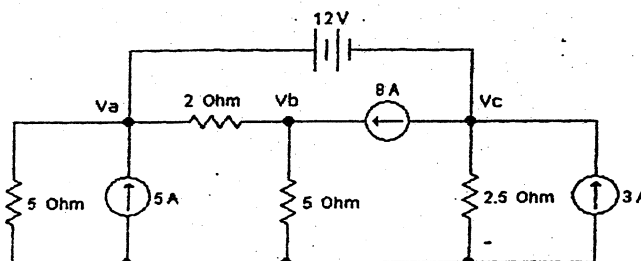- b) Use Nodal Analysis Method to determine the  $V_a$ ,  $V_b$  and  $V_c$  and calculate current through  $2.5\Omega$ . [8]




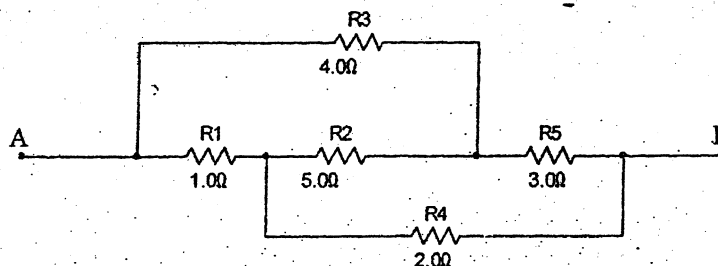3. a) Find the resistance between the terminals A and B in the circuit segment below. [4]






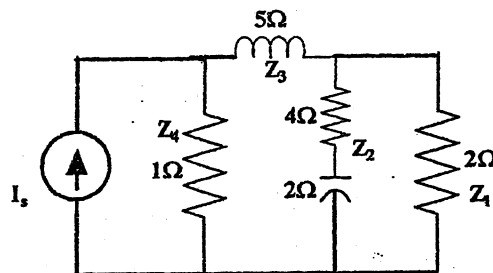- b) Three capacitors A, B and C have capacitances 10, 50 and 25  $\mu\text{F}$  respectively. Calculate: [6]
- Charge on each when connected in parallel to a 250 V supply
  - Total capacitance and
  - p.d. across each when connected in series
- c) State Maximum Power Transfer Theorem and also prove "maximum power will be dissipated when  $R_{\text{internal}} = R_L$ " [6]
4. a) Derive the expression for electrical current in a pure inductive circuit when input power is  $V_m \sin \omega t$ . Draw the wave form of voltage and current and phasor diagram of the circuit. Show analytically and graphically that it does not consume real power. [6]
- b) In the given circuit, find the current through the inductor, what is the equivalent impedance? [6]



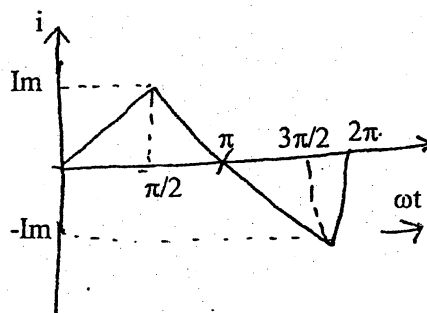- c) Find the peak factor and form factor of the triangular wave shown in figure below. [4]



5. a) Explain the importance of power factor in an ac circuit, with suitable example. How power factor can be improved? [4]
- b) A three phase star connected system with line voltage 400 V is connected to three loads:  $25 \angle 0^\circ$ ,  $11 \angle -20^\circ$  and  $15 \angle 10^\circ$  (also connected in star). Find the line to line current, total power and current in the neutral of the system. [8]
- c) Define phase sequence and explain its significance in three phase system. [4]


\*\*\*

Exam.	New Back (2066 & Later Batch)		
Level	BE	Full Marks	80
Programme	BEL, BEX, BCT, BIE, B.Agr.	Pass Marks	32
Year / Part	I / I	Time	3 hrs.


**Subject:** - Basic Electrical Engineering (EE401)

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt any Five questions.
- ✓ All questions carry equal marks.
- ✓ Assume suitable data if necessary.

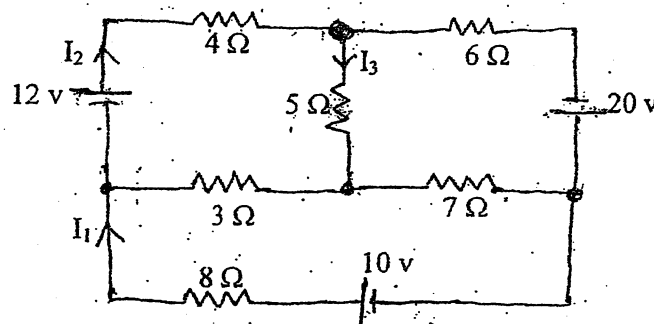
1. a) What is the difference between the potential difference and electromotive force? [4]
- b) Find  $I_1$ ,  $I_2$  and  $I_3$  in the circuit shown in the figure using Kirchhoff's law. [6]



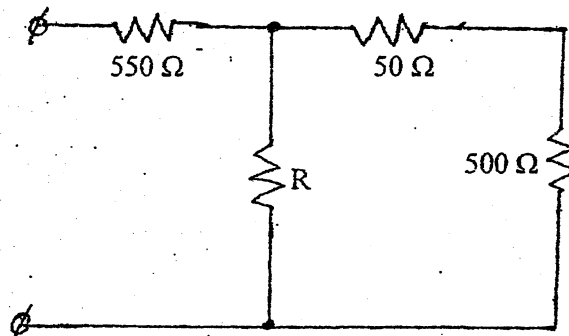
- c) What is the value of the unknown resistor 'R' in figure below, if the voltage drop across  $500\Omega$  resistor is 2.5 volts? [6]



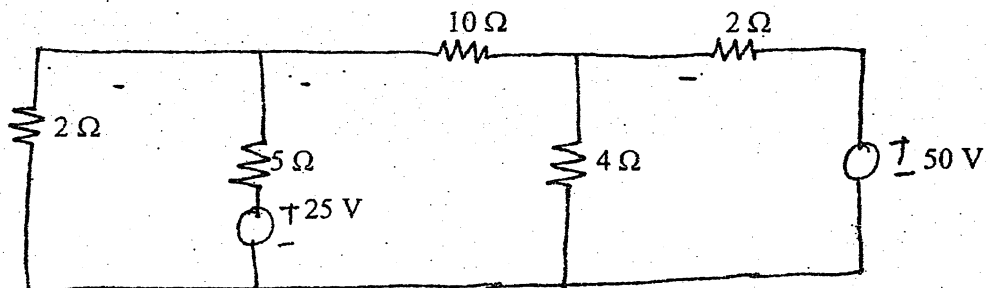2. a) Use the node voltage method (nodal) to find the current flowing through  $10\Omega$  resistor in the network shown figure below. [8]




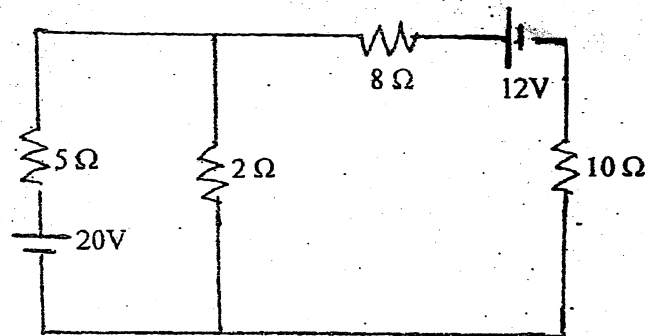- b) For the circuit shown in figure below, calculate the current in the  $10\ \Omega$  resistor using Thevenin's theorem.



3. a) Determine power dissipated in  $3\ \Omega$  resistor in the circuit shown in figure below using Norton's theorem.

[8]

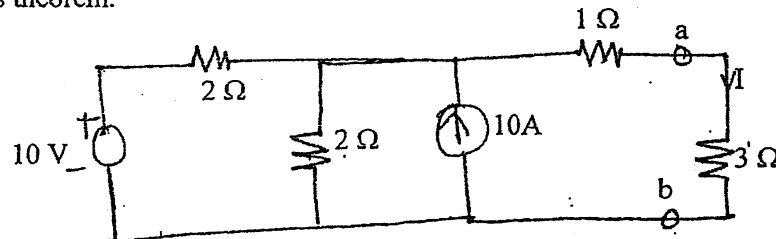

- b) An inductor is to be made with copper wire wound on a circular iron core having mean length of 40 cm with cross-sectional area of 50 sq mm. If the required value of inductance is 500 mH, calculate the number of turns required given that relative permeability of the core is 1500.
4. a) A 415 V, 3 phase, 50 HZ induction motor takes 50 KW power from supply mains at 0.72 power factor lagging. A bank of capacitors is connected in delta across the line to improve the overall power factor. Calculate the capacitance per phase in order to raise the power factor to 0.9 lagging.
- b) Three loads  $(31+j59)\ \Omega$ ,  $(30-j40)\ \Omega$  and  $(80+j60)\ \Omega$  are connected in delta to a 3 phase, 200 V supply. Find the phase currents, line currents and total power absorbed.
5. a) Define cycle, Time period, angular velocity, frequency, average and rms value of an alternating quantity.
- b) A series circuit consists of resistance equal to  $4\ \Omega$  and inductance of 0.01 H. The applied voltage is  $283 \sin(300t + 90^\circ)\text{V}$ . Calculate the following:
- Power factor
  - Expression for  $i(t)$
  - The power dissipated in the circuit
  - Voltage drop across each elements
  - Draw a phasor diagram

[8]

[8]

[8]

[6]

[10]

\*\*\*




Exam.	New Back (2066 & Later Batch)		
Level	BE	Full Marks	80
Programme	BEL, BEX, BCT, BIE, B. Agri.	Pass Marks	32
Year / Part	I / I	Time	3 hrs.


**Subject: - Basic Electrical Engineering (EE401)**

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt ALL questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

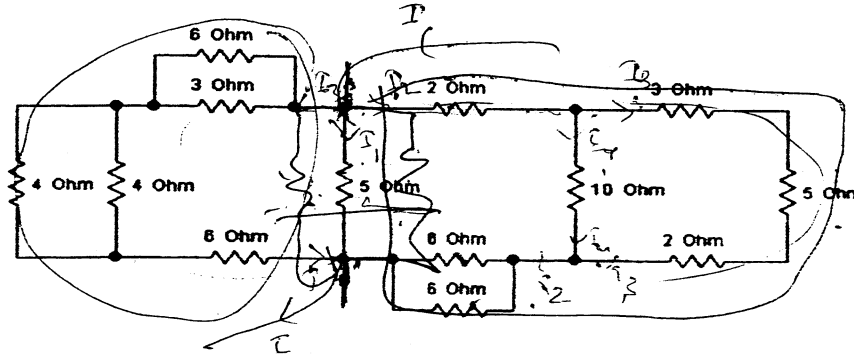1. a) What is the factor responsible for the deviation of the practical sources from their ideal behavior? Explain the effect of this factor on the terminal characteristics of the voltage source. [6]
- b) Write down the steps to calculate Norton's equivalent resistance in the circuit with a suitable example. [4]
- c) A conductor material has a free electron density of  $10^{24}$  electrons per  $m^3$ . When a voltage is applied a constant drift velocity of  $1.5 \times 10^{-2}$  m/s is attained by the electrons. If the cross sectional area of the material is  $1 \text{ cm}^2$ , calculate the magnitude of the current. [6]
2. a) Explain with neat diagram and write the equations for Delta- Star Conversion and for Star-Delta Conversion. [4]
- b) Find the equivalent resistance across the terminals A and B,  $R_{AB}$ . [6]




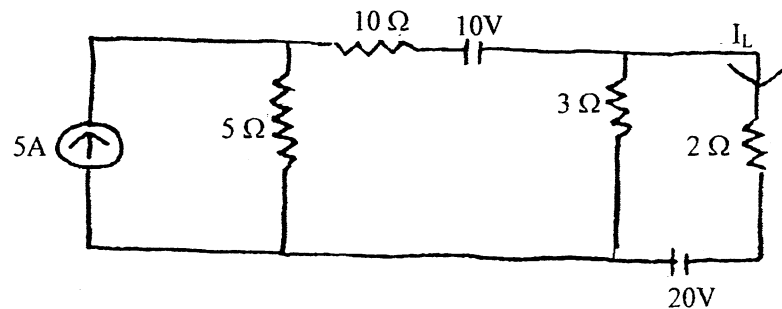- c) "Thevenin's theorem and Norton's theorem are dual of each other". Justify the statement with suitable example. [6]
3. a) Use Superposition theorem to find the current  $I_L$  through  $2 \Omega$  resistors in figure below. [8]




OR

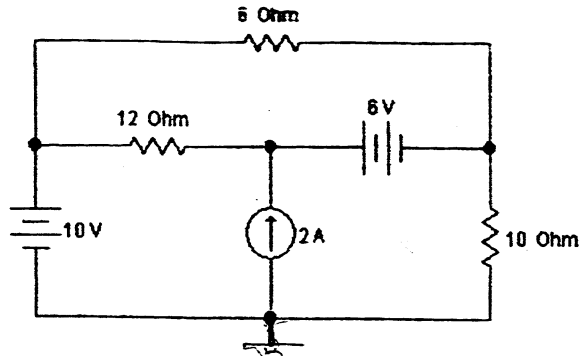Find the current passing through  $10\ \Omega$  resistor using loop current method.




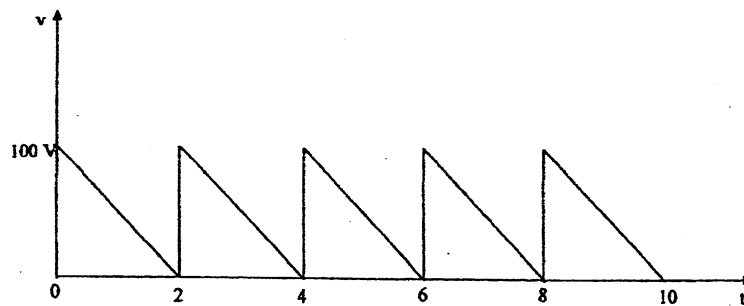- b) Calculate the inductance that must be connected in parallel with a  $100\text{ mH}$  inductor to give a total inductance of  $70\text{ mH}$ . Assume no mutual inductance between the two. [4]
- c) Two impedances  $(3-4j)$  and  $(8+6j)$  are connected in parallel across an ac voltage source. If the total current drawn from the source is  $25\text{ A}$ , find the total active power consumed by the impedances. [4]
4. a) Find the average value, rms value of the voltage waveform given below. [8]



40

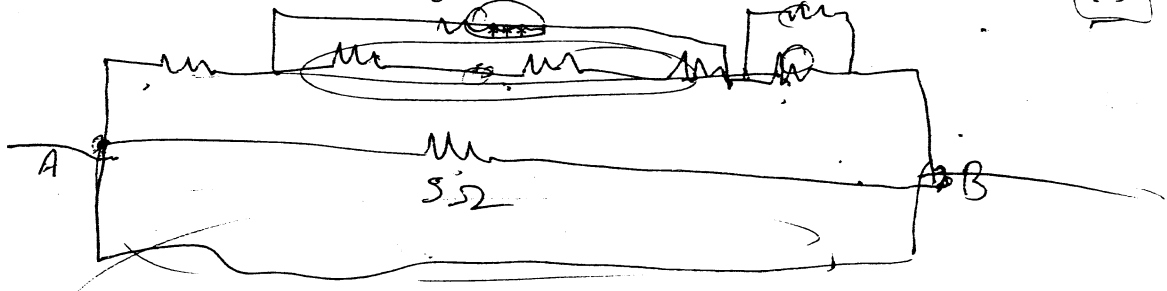- b) An Industrial load consists of the following: [8]
- i) A load of  $200\text{ KVA}$  @  $0.8$  power factor lagging
  - ii) A load of  $50\text{ KW}$  @ unity power factor
  - iii) A load of  $48\text{ KW}$  @  $0.6$  power factor leading
- Calculate the total KW, Total KVAR, Total KVA and the overall power factor.
5. a) A  $100\text{ KW}$  load at  $0.8$  lagging power factor is being supplied by a  $220\text{ V}$ ,  $50\text{ Hz}$  source. Calculate the reactive power drawn from the source. If a capacitor connected parallel to the load improves its power factor to  $0.9$ . Find the capacitance of the capacitor. Also calculate the current drawn from the source before and after connecting the capacitor. [8]
- b) With the help of necessary Phasor diagram and circuit diagram, explain the two wattmeter method of Active Power Measurement in Three Phase AC system? What is the variation of wattmeter readings with load Power Factor? [8]




Exam.	Regular		
Level	BE	Full Marks	80
Programme	BEL, BEX, BCT, BIE, B.Agr.	Pass Marks	32
Year / Part	I / I	Time	3 hrs.


**Subject:** - Basic Electrical Engineering (EE401)

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

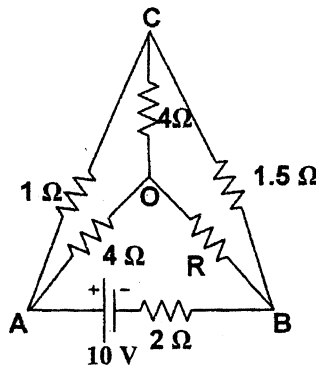
1. a) What do you understand by terms 'resistance' and 'resistivity'? On what factors the resistance offered by a conductor depends? [4]
- b) Two resistors made of different materials having temperature coefficients of resistance  $\alpha_1 = 0.004/^\circ\text{C}$  and  $\alpha_2 = 0.005/^\circ\text{C}$  are connected in parallel and consume equal power at  $15^\circ\text{C}$ . What is the rate of power consumed in resistance  $R_2$  to that in  $R_1$  at  $70^\circ\text{C}$ ? [6]
- c) Calculate the value of unknown resistance  $R$  in the circuit shown below and the current flowing through it when the current in the branch OC is zero. [6]



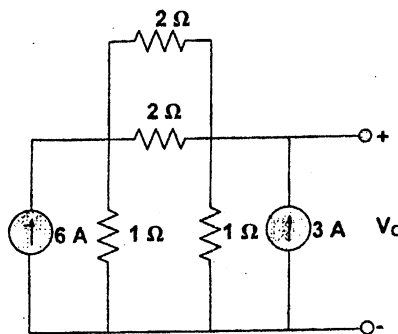2. a) Calculate the output voltage,  $V_o$  for the circuit shown in figure below using Kirchoff's laws. [5]



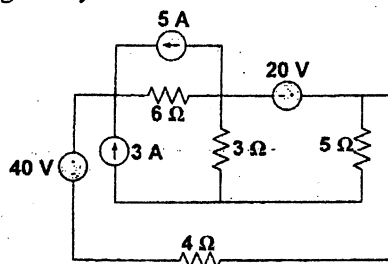
- b) Determine the power dissipated by  $5\Omega$  resistor in the circuit shown in figure below by applying nodal voltage analysis. [6]




- c) State and explain superposition Theorem with an appropriate example. [5]



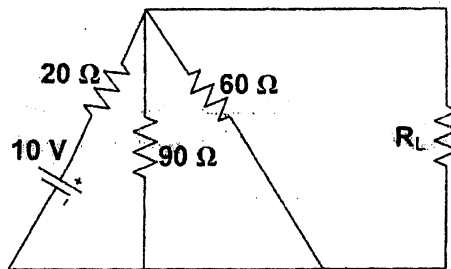3. a) For the circuit shown in figure below, what will be the value of  $R_L$  to get the maximum power? What is the maximum power delivered to the load? [8]



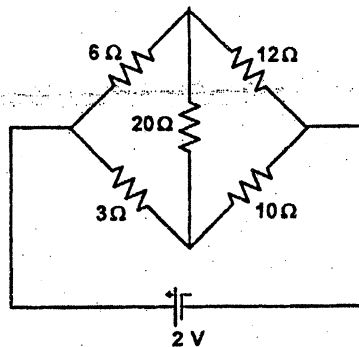- b) Determine the current in  $20\Omega$  resistor of the network shown in figure below using Star Delta Transformation [4]



- c) State the definition of the capacitance and from it write an equation for the charge stored in a capacitor. [4]
4. a) Derive the equation for instantaneous current flowing through a pure capacitor when excited by AC sinusoidal voltage  $V = V_m \sin \omega t$ . Draw the waveform of voltage and current and phasor diagram of the circuit. Show analytically and graphically that it does not consume real power. [4]
- b) A coil takes 1.3 kVA and 1.2 kVAR when connected to a 240 V, 50 Hz sinusoidal supply. Calculate: (i) Power dissipated (ii) Current and (c) Inductance of the coil. [4]
- c) A Circuit consisting of a resistance of  $30\Omega$  in series with an inductance of 75mH is connected in parallel with a circuit consisting of a resistance of  $20\Omega$  in series with a capacitance of  $100\mu\text{F}$ , if the parallel combination is connected to a 240V, 50Hz, single-phase supply. Calculate (i) The total current (ii) Power factor (iii) Active and reactive power. Also draw a neat phasor diagram. [8]
5. a) What are the two ways of connecting a 3-phase system? Draw their phasor diagrams and write down the relationship between phase and line voltages and phase and line current for these system. [4]
- b) A 220 V, 3-phase voltage is applied to a balanced delta connected 3-phase load of phase impedance  $(15+j20)\Omega$ . Calculate: [8]
- The phase voltages
  - The phasor current in each line
  - The power consumed per phase
  - Draw the phasor diagram
  - What is the phasor sum of three line currents? Why does it have this value?
- c) Explain 2-wattmeter method for the measurement of power in a balanced three phase load. [4]


Exam.	Regular		
Level	BE	Full Marks	80
Programme	BEL, BEX, BCT, BIE, B.Agr.	Pass Marks	32
Year / Part	I / I	Time	3 hrs.

**Subject:** - Basic Electrical Engineering (EE401)

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt any **Five** questions.
- ✓ The figures in the margin indicate **Full Marks**.
- ✓ Assume suitable data if necessary.

1. a) Explain the methods for converting practical current source in to practical voltage source. [4]

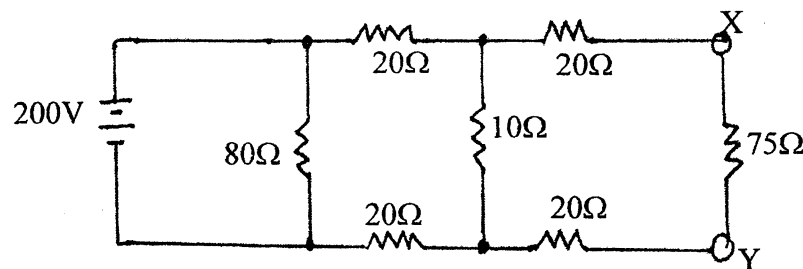b) Calculate the power which would be dissipated in a  $75\ \Omega$  resistor connected across XY in the network shown below. [4]



c) Find the currents  $I_1$ ,  $I_2$ ,  $I_3$  using Kirchhoff's Law and also find the power output of each voltage source of figure below? [8]


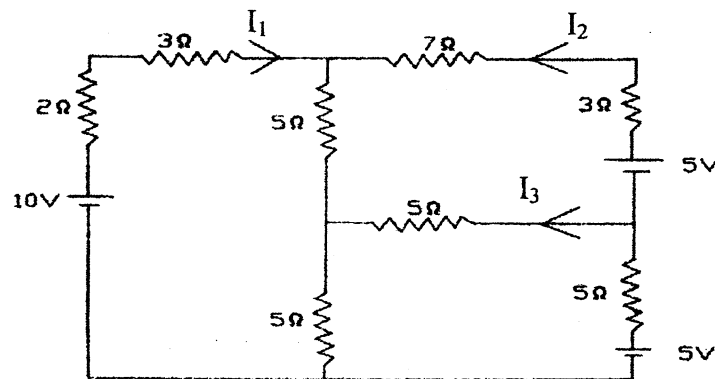


Fig: 1.2

2. a) The resistivity of a metal alloy is  $50 \times 10^{-8}\ \Omega\text{-m}$ . A sheet of material 15 cm long, 6 cm wide and 0.014 cm thick. Calculate the resistance in the direction: (a) along the length and (b) along the thickness. [4]

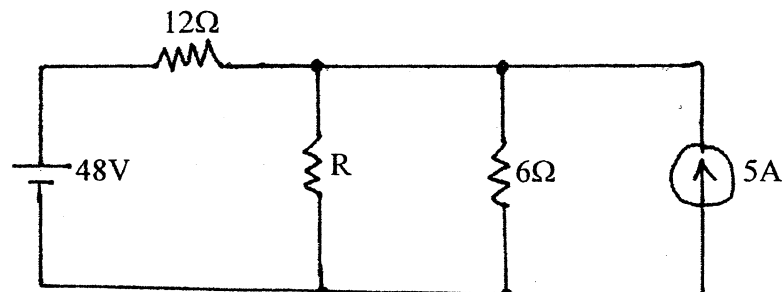
b) Use Norton's theorem to calculate the value of R that will absorb maximum power from the circuit shown in the figure below. Also calculate the maximum power drawn by it. [4]







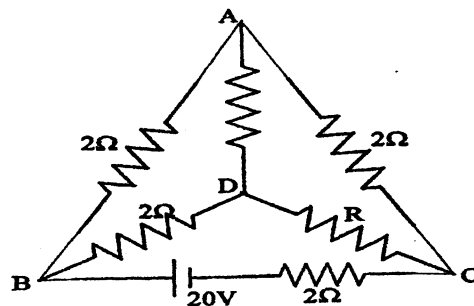- c) In the network shown below, find the value of resistance  $R$  and the current through it when the current through branch  $DA$  is zero. [4]



3. a) Find the current through the  $10\ \Omega$  resistor using loop-current method? [8]


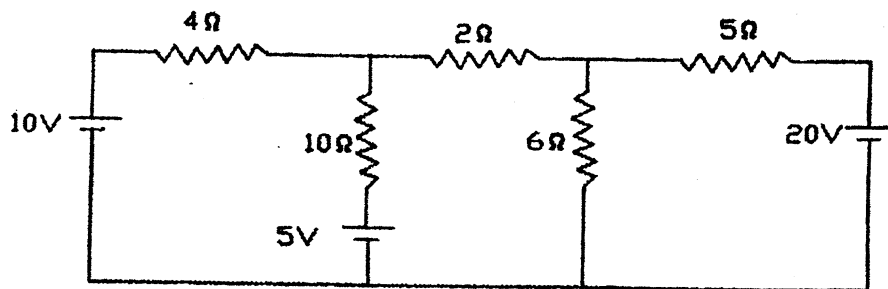


Fig: 3.1

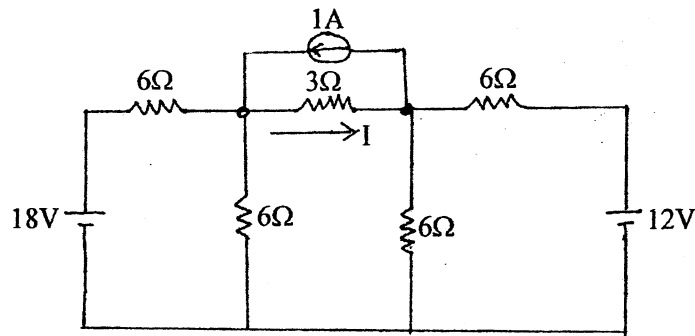- b) Find the current  $I$  in the circuit of figure below by applying nodal voltage method. [8]




- a) Explain generation of sinusoidal emf with diagram and define angular velocity. [6]  
 b) A sinusoidal voltage is applied to three parallel branches yielding branch currents,  $i_1 = 14.14 \sin(\omega t - 45^\circ)$ ,  $i_2 = 28.3 \cos(\omega t - 60^\circ)$  and  $i_3 = 7.07 \sin(\omega t + 60^\circ)$  (i) Find the complete time expression for the source current (ii) Draw the phasor diagram in terms of effective values. Use the voltage as reference. [6]  
 c) Define inductance and derive relation for connection of inductors connected in parallel connection. [4]

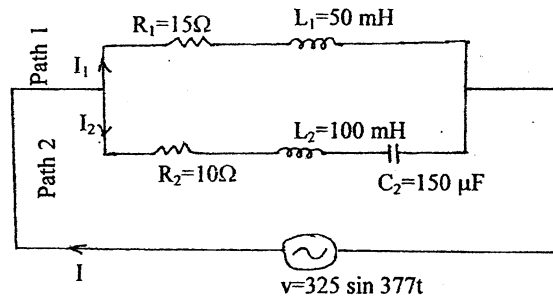5. a) For the parallel circuit shown below, calculate:

[8]

- RMS value for current, power factors and active power of path 1.
- RMS value of current, power factor and reactive power of path 2.
- RMS value of current and power factor of the whole circuit.



- b) A three phase induction motor takes 50KW at 415V, 50Hz and a power factor of 0.72 lagging. Determine the KVAR rating of capacitor bank to improve the power factor to 0.9 lagging. What capacitance per phase is required if the capacitor bank is connected in star connection? What is the advantage of power factor correction from the source point of view and from the point of view of motor itself?

[6+2]

6. a) In the network shown in figure below, determine:

[8]

- Total impedance
- Total current
- The current in each branch
- The overall power factor
- Volt amperes, Active Power and Reactive Power

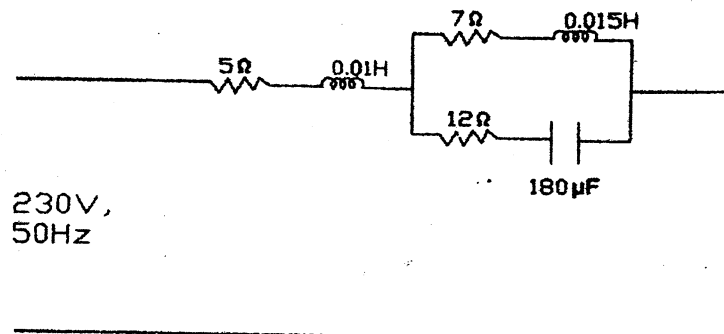


Fig: 5.1

- b) In a 3-phase, 4 wire Wye connected system the phase voltage  $V_{ph} = 200V$ , and its frequency is 60Hz. The load impedance components are  $R_1 = 100\Omega$ ,  $R_2 = 100\Omega$ ,  $C_2 = 66.3 \mu F$ ,  $R_3 = 100\Omega$ ,  $L_3 = 159.2mH$ . Calculate the three line currents and the neutral current.

[8]

\*\*\*

## Examination Control Division


2068 Baishakh

Exam.	Regular / Back		
Level	EE	Pass Marks	32
Programme	BEL, BEX, BCT, BIE, B.Agr	Pass Marks	32
Year / Part	I / I	Time	3 hrs.


**Subject:** - Basic Electrical Engineering

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt any Five questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

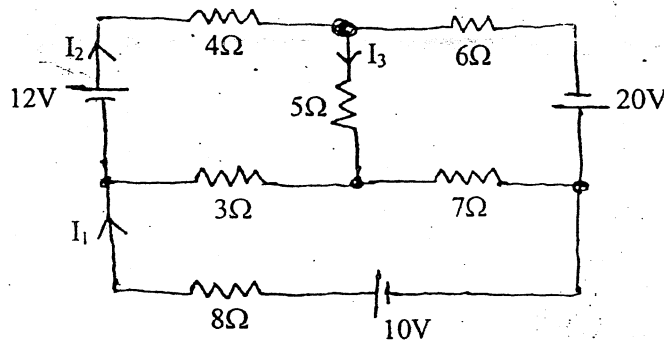
1. a) The temperature rise of a m/c field winding was determined by the measurement of the winding resistance. At 20°C the field resistance was 150Ω. After running the m/c for 6 hours at full load, the resistance was 175Ω. The temperature coefficient of resistance of the copper winding is  $4.3 \times 10^{-3}/^{\circ}\text{C}$ . Determine the temperature rise of the m/c. [6]
- b) Find  $I_1$ ,  $I_2$ , and  $I_3$ , in the circuit shown in the figure using Kirchhoff's law. [10]



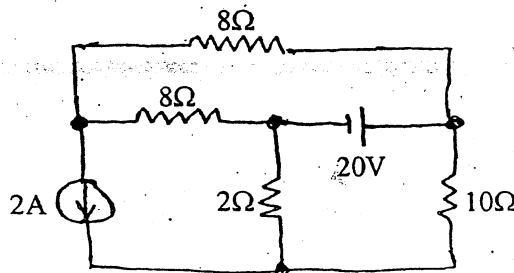2. a) Use Superposition theorem to find the current flowing through the 10Ω resistor shown in the figure. [8]




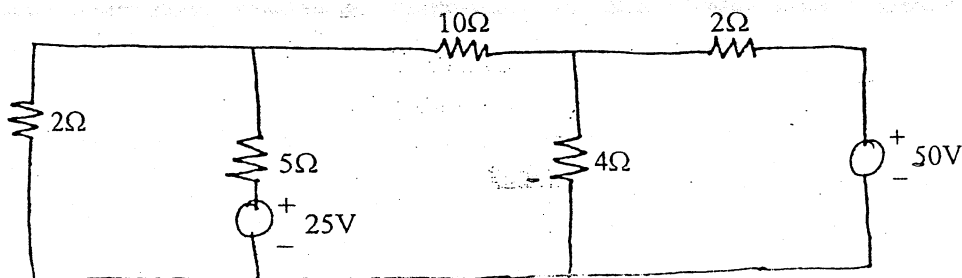- b) State Thevenin's theorem and give the procedure for Thevenizing a circuit. Explain the major advantages offered by use of this theorem. [8]
3. a) Use the node voltage method (Nodal) to find the current flowing through 10Ω resistor in the network shown below. [8]





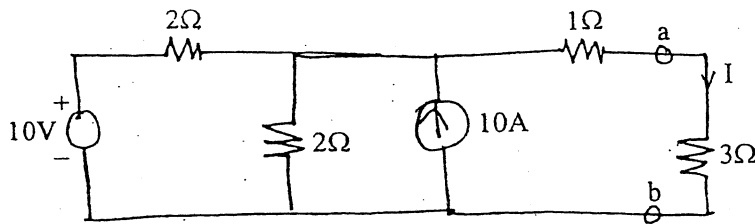
- b) Determine the power dissipated in  $3\Omega$  resistor in the circuit shown below using Norton's thco.em. [8]



4. a) An rms voltage of  $100\angle 0^\circ$  is applied to the series combination of  $\bar{Z}_1$  and  $\bar{Z}_2$  where  $\bar{Z}_1 = 20\angle 30^\circ$ . The effective voltage drop across  $\bar{Z}_2$  is known to be  $40\angle -30^\circ$  V. Find the reactive component of  $\bar{Z}_2$ . [8]

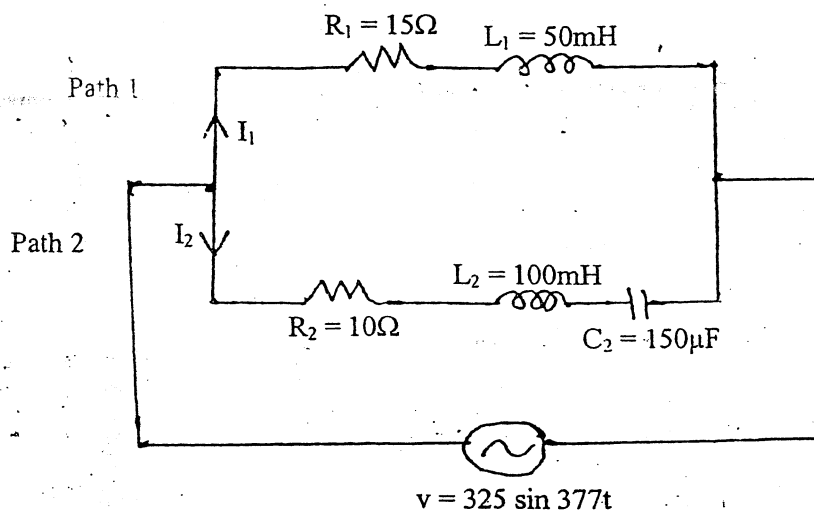- b) For the parallel circuit shown below, calculate: [8]

- RMS value of current, power factor, active and reactive power of path 1
- RMS value of current, power factor, active and reactive power of path 2
- RMS value of current, power factor, active and reactive power of the whole circuit



5. a) Define cycle, Time period, angular velocity, frequency, average and rms value of an alternating quantity. [6]

- b) A series circuit consists of resistance equal to  $4\Omega$  and inductance of  $0.01$  H. The applied voltage is  $283 \sin(300t + 90^\circ)$  V. Calculate the followings: [10]

- Power factor
- Expression for  $i(t)$
- The power dissipated in the circuit
- Voltage drop across each elements and
- Draw a phasor diagram

6. a) A 415V, 3 phase, 50Hz induction motor takes 50kW power from supply mains at 0.72 power factor lagging. Capacitors are connected in delta across the line to improve the overall power factor. Calculate the capacitance per phase in order to raise the power factor to 0.9 lagging. [8]

- b) Three loads  $(31 + j59)\Omega$ ,  $(30 - j40)\Omega$  and  $(80 + j60)\Omega$  are connected in delta to a 3 phase, 200V supply. Find the phase currents, line currents and total power absorbed. [8]

\*\*\*


2068 Chaitra

Exam.	Level	Programme	Year / Part	Full Marks	Pass Marks	Time
	BE	BEL, BEX, BCT, BIE, B. Agri.	1 / 1	80	32	3 hrs.


**Subject: - Basic Electrical Engineering (EE 401)**

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt any Five questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

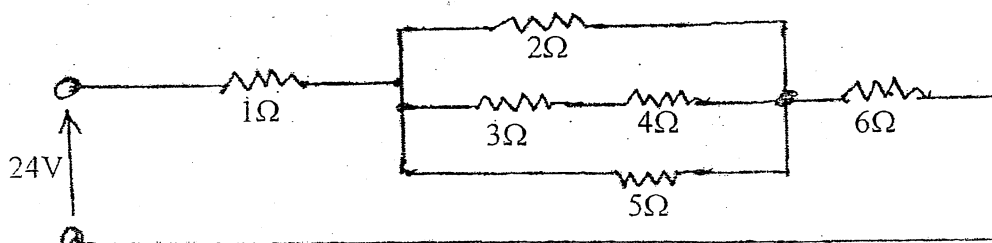1. a) Explain emf, potential difference and current with a circuit diagram. [4]
- b) The temperature rise of the machine field winding was determined by the measurement of the winding resistance at 20°C the field winding resistance was 160 Ohm( $\Omega$ ). After running the machine for some hours at full load the resistance is 185  $\Omega$ . If the temperature coefficient of resistance of the copper winding is  $4.3 \times 10^{-6}/^{\circ}\text{C}$  at 0°C. Determine the temperature rise of the machine. [6]
- c) Find the equivalent resistance in the figure shown, and power dissipated in the 5 $\Omega$  resistor. [6]



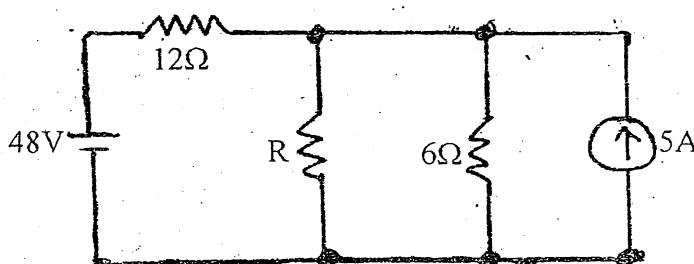
2. a) Calculate the value of R that will absorb maximum power from the circuit (shown in the figure). Also calculate the maximum power drawn by it. [6]




- b) State Norton's description theorem and list the steps for Nortonizing a circuit. Compare the Norton's equivalent circuit to the Thevenin's equivalent circuit. [6]
- c) What is the total cost of using the following at Rs 7 per kallowatt hour? [4]
  - i) A 1200 W toaster for 30 min
  - ii) Six 50 W bulbs for 4 hours

- iii) A 400 W washing machine for 45 min.  
iv) A 4800 W electric cloths dryer for 20 min.

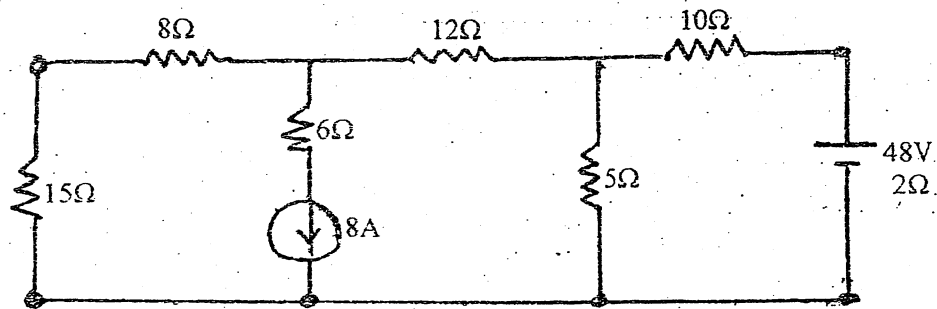
3. a) Use Nodal analysis method to calculate the current through the  $15\Omega$  resistor in the figure shown below. [8]



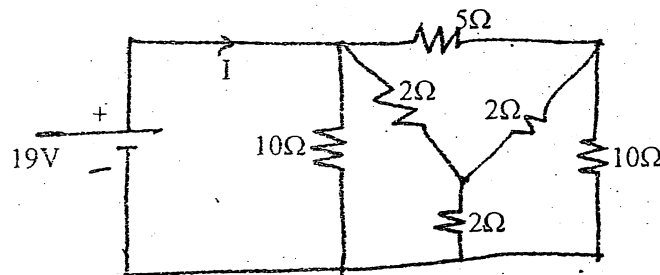- b) Find the current  $I$  as shown in figure below using star - delta transformation. [4]



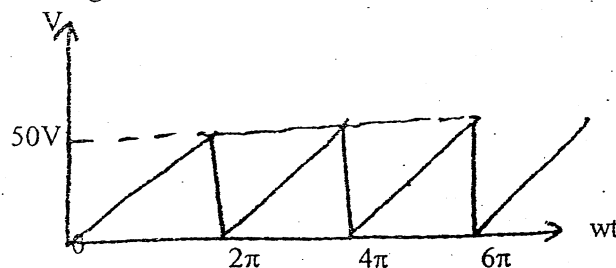
- c) An air cored coil is 2.5cm long and has an average cross-sectional area of  $2\text{cm}^2$ . Determine the number of turns if the coil has an inductance of  $100\mu\text{H}$ . [4]  
4. a) Calculate the average value, rms value, form factor and peak factor of the saw tooth wave as shown in figure below. [6]



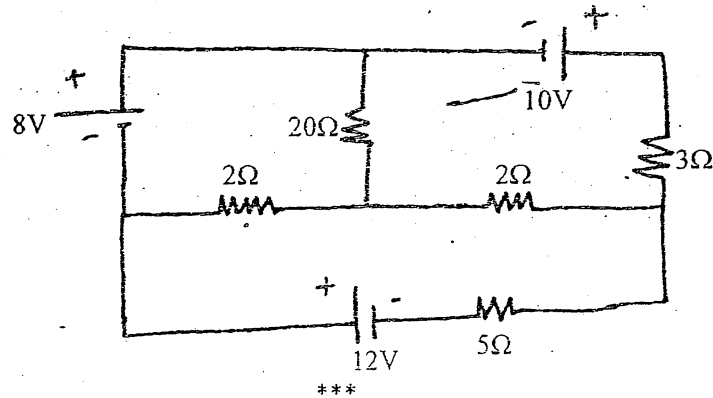- b) What do you mean by reactive power in AC circuit? Explain it by constructing phasor diagram for real power, reactive power and apparent power. [5]  
c) Describe and illustrate the phasor relationship that exist between the voltage that appears across the terminals of a pure capacitor and the current that flows through it in steady state when the capacitor is excited by a sinusoidal source. [5]  
5. a) A voltage of  $200\angle 0^\circ\text{ V}$  is applied across impedances in parallel. The value of impedances are  $(12 + j16)\Omega$  and  $(10 - j20)\Omega$ . Determine the KW, KVA and KVAR in each branch and the power factor of the whole circuit. [8]  
b) A delta connected load of  $Z_{AB} = 52\angle 45^\circ\Omega$ ,  $Z_{BC} = 52\angle -30^\circ\Omega$  and  $Z_{CA} = 10\angle 0^\circ\Omega$  are connected to a 380V, 3 phase ac source. Find the magnitude of the line currents and total power absorbed by loads, when phase sequence is ABC. [8]



- [8] a) A single phase motor takes a current of 40A at pf 0.7 lagging from a 440V, 50HZ supply. What value must a shunting capacitor have to raise the power factor to 0.9 lagging. [6]
- b) What are the advantages of three phase AC system over single phase ac system? [4]
- c) Determine current in  $5\Omega$  resistor by mesh analysis in figure below. [6]





25 TRIBHUVAN UNIVERSITY  
INSTITUTE OF ENGINEERING  
**Examination Control Division**


2067 Ashadh

Exam.	Regular/Back		
Level	BE	Full Marks	80
Programme	BEL, BEX, BCT, BIE, B.Agric.	Pass Marks	32
Year / Part	I / I	Time	3 hrs.


**Subject: - Basic Electrical Engineering**

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt any **Five** questions.
- ✓ **All** questions carry equal marks.
- ✓ Assume suitable data if necessary.

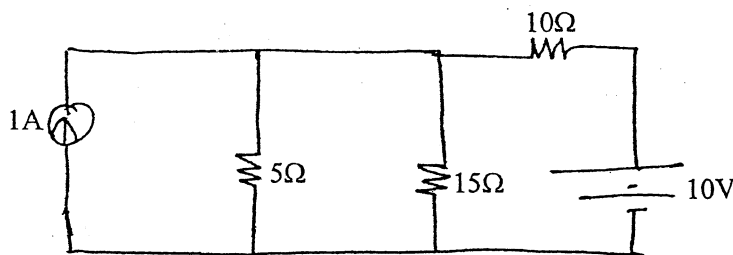
1. a) The temperature rise of the machine field winding was determined by the measurement of the winding resistance. At  $20^{\circ}\text{C}$  the field resistance was  $150\ \Omega$ . After running the m/c for 6 hours at full load, the resistance was found to be  $175\ \Omega$ . If the temperature coefficients of resistance of the copper winding is  $1.57 \times 10^{-5}/^{\circ}\text{C}$  at  $0^{\circ}\text{C}$ , determine the temperature rise of the machine.
- b) What are ideal and practical voltage and current sources? Explain.
2. a) Calculate the current in the  $15\ \Omega$  resistor in the network shown in figure below using superposition theorem.



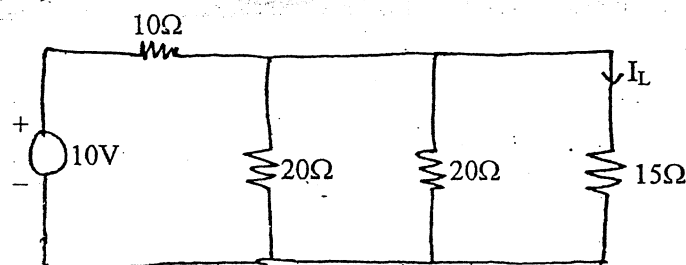- b) Determine the current  $I_L$  through  $15\ \Omega$  resistor in the network by Norton's theorem.




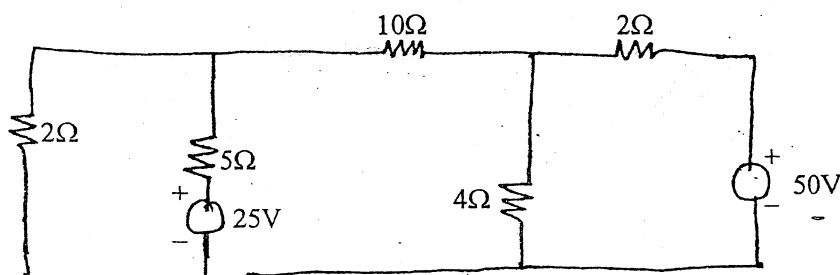3. a) Use nodal method to find the current through  $10\ \Omega$  resistor for circuit shown below.






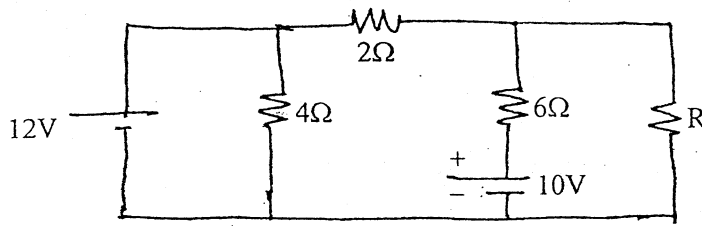- b) Calculate the value of  $R$  to receive maximum power and the maximum power received by it for the circuit shown below.



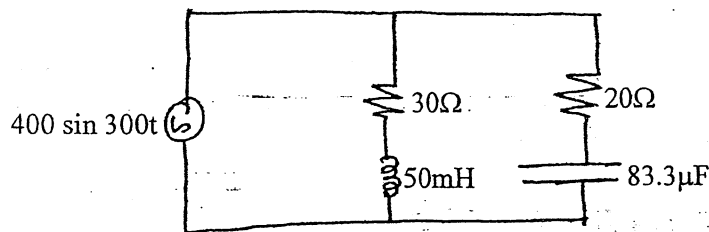4. a) A series circuit consists of a resistance equal to  $4\Omega$  and inductance of  $0.01\text{H}$ . The applied voltage is  $v = 283 \sin(300t + 90^\circ)$  volts. Find
- The power dissipated in the circuit
  - The expression for  $i(t)$
  - Power factor and
  - Draw a phasor diagram
- b) For the circuit below, calculate
- Magnitude and phase angles of current in each of the branches,
  - Active, reactive and apparent power and power factor of the circuit, and
  - Draw the vector diagram indicating branch currents and supply voltage



5. a) Describe the advantages of three phase AC system over single-phase AC system.
- b) Three phase balanced load consists of three similar coils, each of resistance  $50\Omega$  and inductance of  $0.3\text{H}$ . The supply voltage is  $415\text{V}$ ,  $50\text{Hz}$ . Calculate (i) The line current (ii) The power factor (iii) Total power consumed and (iv) Draw the phasor diagram. Take R×B as phase sequence.
6. a) Define power factor and explain the disadvantages and causes of low power factor?
- b) A single-phase  $50\text{Hz}$  motor takes  $20\text{A}$  at  $0.65$  power factor lagging from a  $230\text{V}$  sinusoidal supply. Calculate the KVar rating and capacitance to be connected in parallel to raise the power factor to  $0.9$  lagging. What is the new supply current?

\*\*\*


TRIBHUVAN UNIVERSITY  
INSTITUTE OF ENGINEERING  
**Examination Control Division**  
2075 Chaitra

Exam.	Regular / Back		
Level	BE	Full Marks	80
Programme	BEL, BEX, BEI, BCT, BAM, BIE, BAG, BAS	Pass Marks	32
Year / Part	I / I	Time	3 hrs.


**Subject: - Basic Electrical Engineering (EE 401)**

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

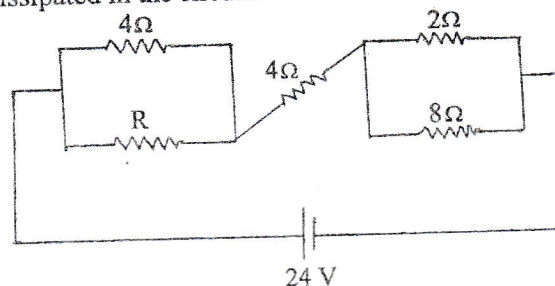
1. a) Discuss on brief voltage and current sources. Also justify the statement "terminal voltage goes on increasing on decreasing load current". [4]
- b) The resistance of the certain length of wire is 4.60 ohm at 20°C and 5.68 ohm at 80°C. Determine (i) the temperature coefficient of resistance of the wire at 0°C, (ii) the resistance of the wire at 60°C. [6]
- c) State and explain Kirchoff's current laws. Determine the value of unknown resistance R and the total current drawn from the source in the circuit of figure. Also compute the total power dissipated in the circuit. [6]



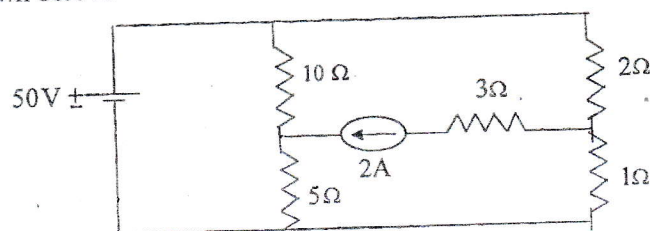
2. a) Use loop current method to calculate the current through the 5 Ω resistance for the network shown below. [8]



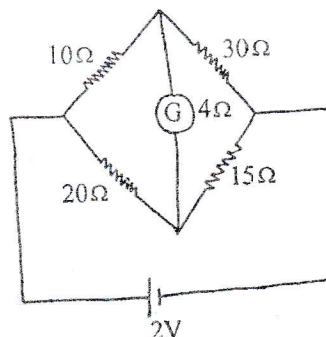
- b) Using delta/star transformation, find the galvanometer current in the Wheatstone bridge. [8]



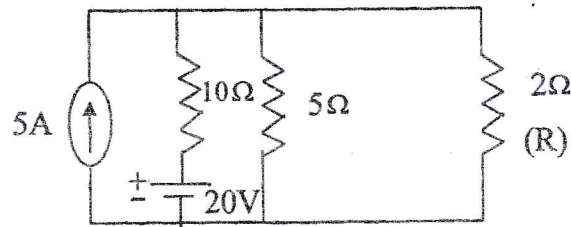3. a) Find the current through R using thevenin's theorem. Also, find the value of R such that maximum power transfer takes place from the source to R in the network shown below. [8]



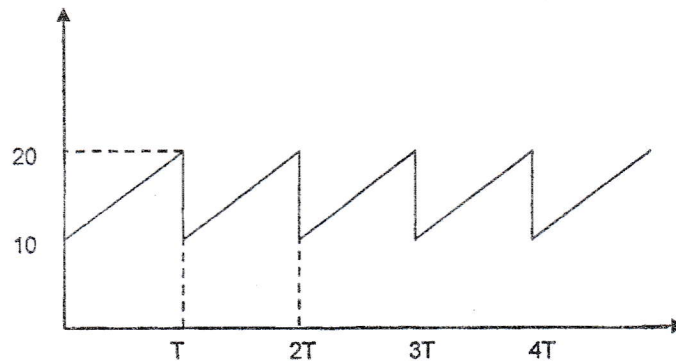- b) Derive an expression for the equivalent capacitance of a group of capacitors when they are connected in series. [4]  
 c) Calculate the form factor and peak factor of the following waveform. [4]



4. a) State and explain Norton's theorem with a suitable example. [4]  
 b) A resistance of  $12\ \Omega$ , an inductance of  $0.15\ \text{H}$  and a capacitance of  $130\ \mu\text{F}$  are connected in series across a  $100\text{V}$ ,  $50\text{Hz}$  supply. Calculate the impedance, current and phase angle and power factor. [4]  
 c) A parallel circuit consists of two branches, one containing a coil of resistance  $5\ \Omega$  and inductance  $38.2\text{mH}$ , the other a non-inductive resistance  $16\ \Omega$  in series with a capacitor of  $300\ \mu\text{F}$  capacitance. The circuit is connected to a  $240\ \text{V}$ ,  $50\ \text{Hz}$  supply. Determine (i) the current in each branch (ii) the total current (iii) the circuit phase angle (iv) the circuit impedance (e) the components of an equivalent circuit consisting of a resistance and reactance. [8]  
 5. a) Define power factor and explain causes of low factor. A single phase  $240\text{V}$ ,  $50\ \text{Hz}$  induction motor takes  $20\text{A}$  at power factor of  $0.75$  lagging. It is desired to raise the power factor to  $0.95$  lagging by connecting a capacitor across the load. Calculate the capacitance of the capacitor to be used in parallel with induction motor. [2+6]  
 b) A three phase  $400\ \text{V}$ ,  $50\ \text{Hz}$  power line has two loads connected to it. The first is delta-connected and draws  $25\ \text{Kw}$  at  $0.70$  power factor lagging. The second is wye-connected and draws  $6.25\ \text{kVA}$  at  $0.8$  power factor leading. What is the total line current and the combined power factor. [8]

\*\*\*




TRIBHUVAN UNIVERSITY  
 INSTITUTE OF ENGINEERING  
**Examination Control Division**  
 2076 Ashwin

Exam.	Back		
Level	BE	Full Marks	80
Programme	BEL, BEX, BEI, BCT, BAM, BIE, BAG, BAS	Pass Marks	32
Year / Part	I / I	Time	3 hrs.


**Subject: - Basic Electrical Engineering (EE 401)**

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

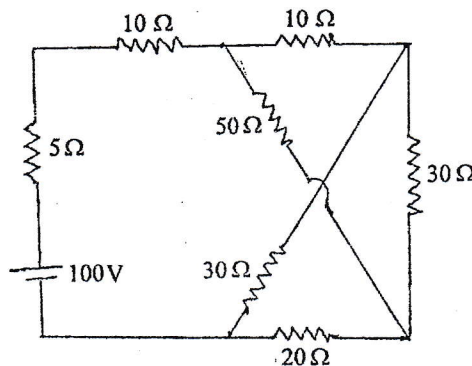
1. a) What are ideal and practical voltage and current source? Explain. [4]
- b) A coil has a resistance of  $18\ \Omega$  when its mean temperature is  $20^\circ\text{C}$  and of  $20\ \Omega$  when its mean temperature is  $50^\circ\text{C}$ . Find its mean temperature rise when its resistance is  $21\ \Omega$  and the surrounding temperature is  $15^\circ\text{C}$ . [6]
- c) State and explain Kirchoff's voltage laws. Determine the current supplied by the battery in the circuit shown in figure below. [6]



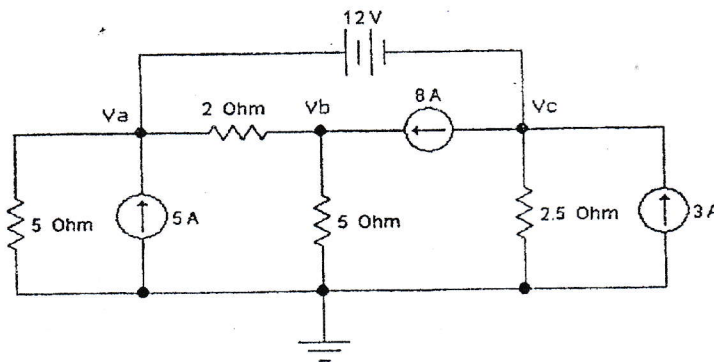
2. a) Use Nodal Analysis Method to determine the  $V_a$ ,  $V_b$  and  $V_c$  and Calculate current through  $2\ \Omega$ . [8]



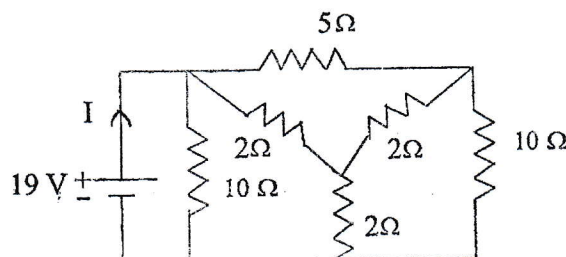
- b) Find the current  $I$  as shown in figure using star – delta transformation. [8]



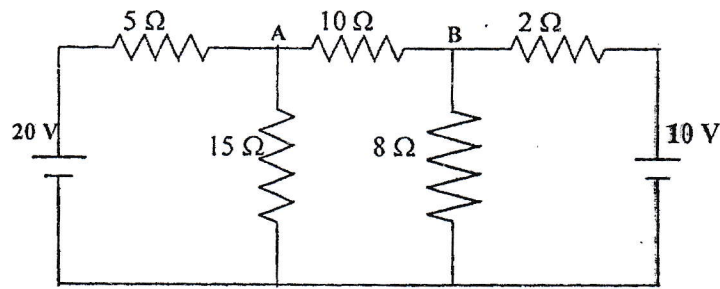3. a) Calculate the current in the  $10\Omega$  resistor in the networks shown in the circuit using Thevenin's Theorem. [8]



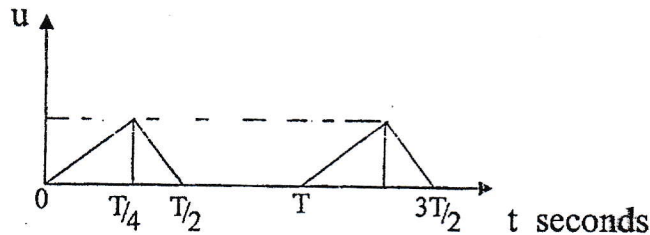- b) Explain what is mean by self inductance and mutual inductance of a coil. [4]  
 c) Calculate the average and rms value of the waveform shown below, over one cycle. [4]



4. a) State and explain reciprocity theorem with a suitable example. [4]  
 b) A resistance of  $20\Omega$ , an inductance of  $0.2\text{ H}$  and a capacitance of  $100\text{ }\mu\text{F}$  are connected in series across a  $220\text{ V}$ ,  $50\text{ Hz}$  supply. Determine the following (i) impedance (ii) current (iii) voltage across R, L and C. [4]  
 c) Two impedances  $z_1$  and  $z_2$  are connected in parallel. The first branch takes a leading current of  $16\text{ A}$  and has a resistance of  $5\Omega$ , while the second branch takes a lagging current at power factor  $0.8$ . The total power supplied is  $5\text{ kW}$ , the applied voltage being  $(100+j200)\text{ V}$ . Determine the branch and total currents. [8]  
 5. a) What are the disadvantages of supplying a low power factor? A  $100\text{ KW}$  load at  $0.85$  lagging power factor is being supplied by a  $230\text{ V}$ ,  $50\text{ Hz}$  source. Calculate the reactive power drawn from the source. If a capacitor connected parallel to the load improves its power factor to  $0.9$ , find the capacitance of the capacitor. Also, calculate the current drawn from the source before and after connecting the capacitor. [2+6]  
 b) A three phase delta connected system with  $400\text{ V}$  line voltage is connected to three unbalanced loads:  $(12-j16)\Omega$ ,  $(3+j4)$ , and  $20\Omega$ , are also connected in delta. Find (i) phase currents (ii) line currents (iii) total active power consumed. [8]

\*\*\*

TRIBHUVAN UNIVERSITY  
INSTITUTE OF ENGINEERING  
**Examination Control Division**


2076 Chaitra

Exam.	Regular		
Level	BE	Full Marks	80
Programme	BEL, BEX, BEL, BCT, BAM, BIE, BAG, BAS, BCH	Pass Marks	32
Year / Part	I / I	Time	3 hrs.


**Subject: - Basic Electrical Engineering (EE 401)**

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.

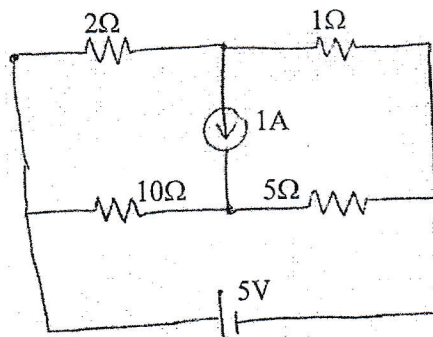
1. a) What do you mean by ideal and practical voltage source? Explain the effect of an internal resistance of voltage and current sources on their terminal characteristics. [4+4]
- b) Using loop current method, determine the current through  $5\Omega$  resistor in the circuit below. [8]



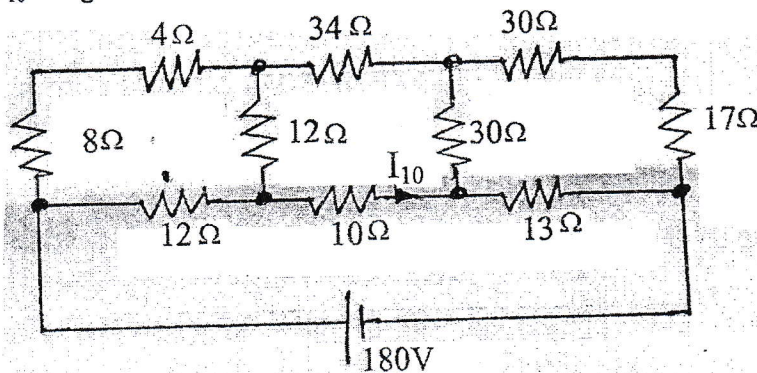2. a) Find the  $I_{10}$  using Y/ $\Delta$  transformation method, in the network given below. [8]




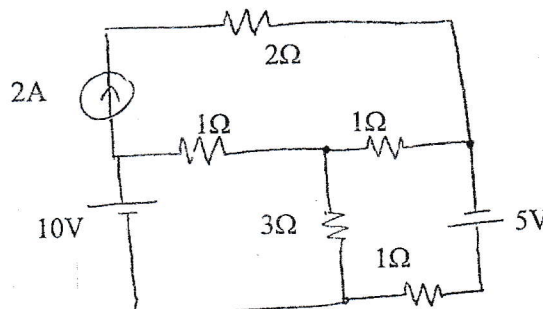- b) Find the current through  $3\Omega$  resistor using Thevenin's theorem. [8]






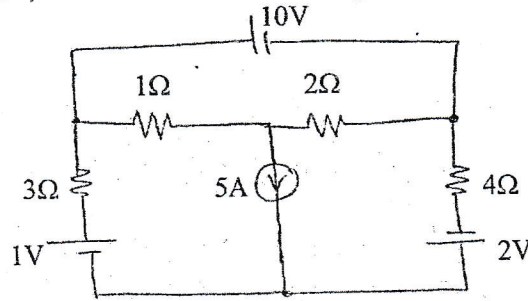3. a) Using Nodal analysis, determine the current through  $2\Omega$  resistor in the circuit below. [8]



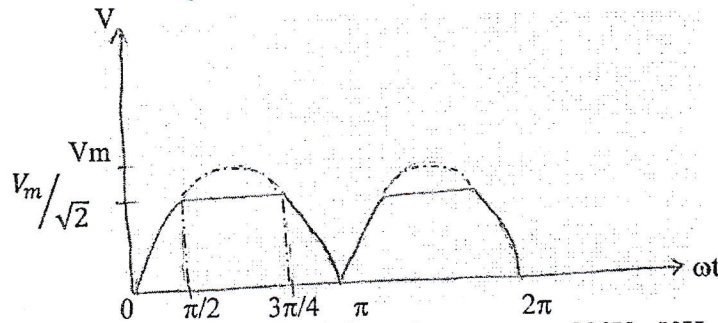- b) What is a self inductance? Derive the expression of equivalent inductance, when the two inductances are connected in series (opposing). [4]
- c) "The average power over complete cycle in a purely inductive circuit is zero". Justify with necessary waveforms and mathematical expression. [4]
4. a) Find the rms and average value of the following waveform. [8]



- b) Two coils A & B are connected in series across a 230V, 50Hz ac supply. The resistance and inductance of coil A & B are  $5\Omega$  and  $0.018H$  respectively. The input from the supply is 2KW and 2kVAR, find the inductance of coil A and resistance of coil B. Also calculate the voltage across each coil. [8]
5. a) A two wattmeters measured an input power of 30KW and 40KW respectively to a motor. If the power factor of the motor be changed to 0.85 leading, determine the two wattmeter readings. The total input power remains the same. Draw a phasor diagram for the second condition. [8]
- b) Three loads  $4-3j$ ,  $6+8j$ , and  $8+6j$  are connected in delta to a 3-phase, 400V supply. Find phase currents, line currents and total power consumed. [8]

\*\*\*